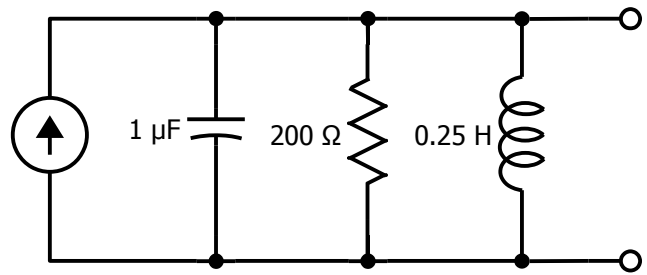


EE3 Fall 2020  
Homework Problem 5


Nhat Ho  
105 355 311

If we are trying to find the Thévenin Equivalent circuit, the easy part is  $V_{th}$ .

- If  $\omega = 1000$  rad/s, what is  $Z_{th}$ ?
- If  $\omega = 2000$  rad/s, what is  $Z_{th}$ ?
- If  $\omega = 4000$  rad/s, what is  $Z_{th}$ ?



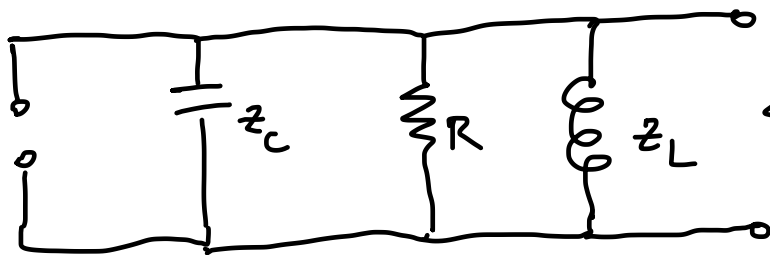To find  $Z_{th}$ , we open circuit for independent current source, we have:



$$\begin{cases} R = 200 \Omega \\ L = 0.25 H \\ C = 1 \mu F \end{cases}$$

$$\Rightarrow Z_{th} = Z_c \parallel R \parallel Z_L = \frac{Z_c R}{R + Z_c} \parallel Z_L$$

$$= \frac{\frac{Z_c R}{R + Z_c} \cdot Z_L}{\frac{Z_c R}{R + Z_c} + Z_L} = \frac{Z_c R Z_L (R + Z_c)}{(R + Z_c) (Z_c R + Z_L (R + Z_c))} = \boxed{\frac{R Z_c Z_L}{R Z_c + R Z_L + Z_L Z_c}}$$

a)  $\omega = 1000$  rad/s,  $R = 200 \Omega$ ,  $L = 0.25 H$ ,  $C = 1 \mu F = 10^{-6} F$

We have:  $Z_L = j\omega L = j \times 1000 \text{ rad/s} \times 0.25 H$

$$\Rightarrow Z_L = 250j (\Omega)$$

$$Z_c = \frac{-j}{\omega C} = \frac{-j}{1000 \times 1 \times 10^{-6} F} = -1000j (\Omega)$$

$$Z_{th} = \frac{R Z_C Z_L}{R Z_C + R Z_L + Z_C Z_L} =$$

$$= \frac{200 \times (-1000j) \times 250j}{200 \times (-1000j) + 200 \times 250j + (-1000j) \times 250j}$$

$$= \frac{50 \times 10^6}{250000 - 150000j} = 147.06 + 88.24j (\Omega)$$

$$= 171.5 \angle 30.96^\circ (\Omega)$$

$$\Rightarrow Z_{th} = 147.06 + 88.24j (\Omega) \\ = 171.5 \angle 30.96^\circ (\Omega)$$

$$b) \omega = 2000 \text{ rad/s}, R = 200 \Omega, L = 0.25 \text{ H}, C = 10^{-6} \text{ F}$$

$$\Rightarrow Z_L = j\omega L = j \times 2000 \times 0.25 = 500j (\Omega)$$

$$\Rightarrow Z_C = \frac{-j}{\omega C} = \frac{-j}{2000 \times 10^{-6} \text{ F}} = -500j (\Omega)$$

$$\Rightarrow Z_{th} = \frac{R Z_C Z_L}{R Z_C + R Z_L + Z_C Z_L}$$

$$\Rightarrow Z_{th} = \frac{200 \times (-500j) \times (500j)}{200 \times (-500j) + 200 \times 500j + 500j \times (-500j)}$$

$$\Rightarrow Z_{th} = \frac{50 \times 10^6}{250 \times 10^3} = \boxed{200 \, (\Omega)}$$

c)  $\omega = 4000 \, (\text{rad/s})$ ,  $R = 200 \, \Omega$ ,  $L = 0.25 \, \text{H}$ ,  
 $C = 1 \, \mu\text{F} = 10^{-6} \, \text{F}$

$$\Rightarrow Z_L = j\omega L = j \times 4000 \times 0.25 = 1000j \, (\Omega)$$

$$\Rightarrow Z_C = \frac{-j}{\omega C} = \frac{-j}{4000 \times 10^{-6} \, \text{F}} = -250j \, (\Omega)$$

$$\Rightarrow Z_{th} = \frac{R Z_C Z_L}{R Z_C + R Z_L + Z_C Z_L}$$

$$= \frac{200 \times (-250j) \times 1000j}{200 \times (-250j) + 200 \times 1000j + 1000j \times (-250j)}$$

$$= \frac{50 \times 10^6}{250 \cdot 10^3 + 150 \cdot 10^3 j} = 147.06 - 88.24j \, (\Omega)$$

$$= 171.5 \angle -30.96^\circ \, (\Omega)$$

$$\Rightarrow \boxed{Z_{th} = 147.06 - 88.24j \, (\Omega) = 171.5 \angle -30.96^\circ \, (\Omega)}$$