

EE3 Fall 2020  
Homework Problem 8

Find the Thévenin  
Equivalent of this circuit.

