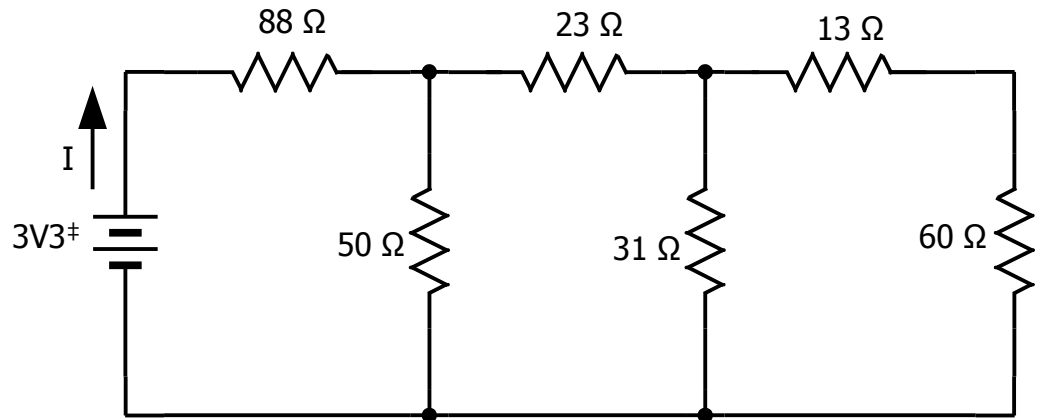


ECE3 Fall 2020

Practice Problems 2

1. This is the problem from Practice Problems 1. Using Node Voltage Analysis, determine the current I.



V_1 : top of 50 Ω resistor

V_2 : top of 31 Ω resistor

$$\frac{V_1 - 3.3}{88} + \frac{V_1}{50} + \frac{V_1 - V_2}{23} = 0$$

$$\frac{V_2 - V_1}{23} + \frac{V_2}{31} + \frac{V_2}{73} = 0$$

$$1150 V_1 - 1150 \cdot 3.3 + 88 \cdot 23 V_1 + 4400 V_1 - 4400 V_2 = 0$$

$$31 \cdot 73 V_2 - 31 \cdot 73 V_1 + 23 \cdot 73 V_2 + 23 \cdot 31 V_2 = 0$$

$$\begin{bmatrix} 1150 + 88 \cdot 23 + 4400 & -4400 \\ -31 \cdot 73 & 31 \cdot 73 + 23 \cdot 73 + 23 \cdot 31 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} 1150 \cdot 3.3 \\ 0 \end{bmatrix}$$

$$V_1 = 0.70 \text{ V}$$

$$V_2 = 0.34 \text{ V}$$

‡ 3V3 is shorthand for 3.3 V. You will see this often on schematics.


ECE3 Fall 2020

Practice Problems 2

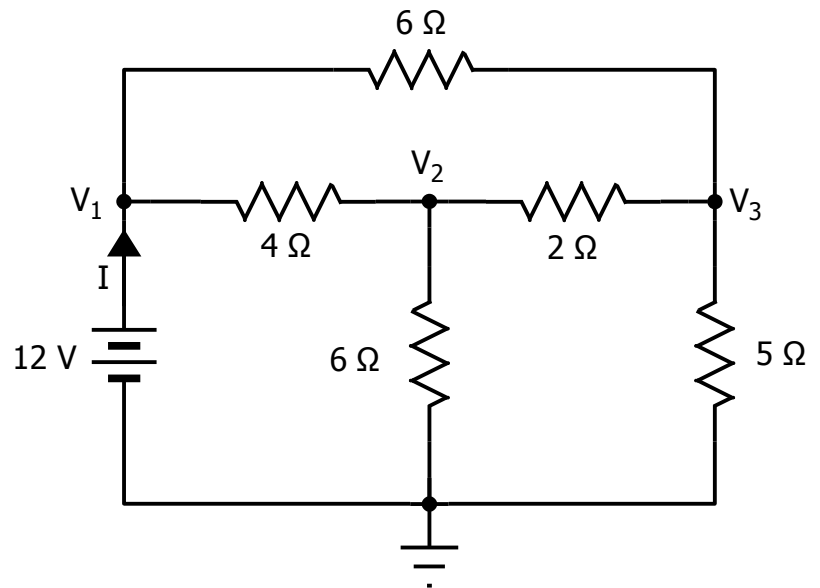2. This is the problem from Lecture 2.

Using Node Voltage Analysis, V_1 , V_2 , and V_3 .

Then find the current through the battery.



$$\text{Node } V_1: V_1 = 12 \text{ V}$$

$$\text{Node } V_2: \frac{V_2 - 12}{4} + \frac{V_2 - 0}{6} + \frac{V_2 - V_3}{2} = 0$$

$$\text{Node } V_3: \frac{V_3 - 12}{6} + \frac{V_3 - V_2}{2} + \frac{V_3}{5} = 0$$

$$3V_2 + 2V_2 + 6V_2 - 6V_3 = 36$$

$$5V_3 + 15V_3 + 6V_3 - 15V_2 = 60$$

$$\begin{bmatrix} 11 & -6 \\ -15 & 26 \end{bmatrix} \begin{bmatrix} V_2 \\ V_3 \end{bmatrix} = \begin{bmatrix} 36 \\ 60 \end{bmatrix}$$

$$V_2 = 6.61 \text{ V}$$

$$V_3 = 6.12 \text{ V}$$

KCL @ V_1 :

$$\frac{V_1 - V_2}{4} + \frac{V_1 - V_3}{6} - I = 0$$

$$I = 2.33 \text{ A}$$

ECE3 Fall 2020


Practice Problems 2

3. This is the same circuit as Problem 2. The reference node has moved.

Using Node Voltage Analysis, find V_1 , V_2 , and V_3 .

Then find the current through the battery.

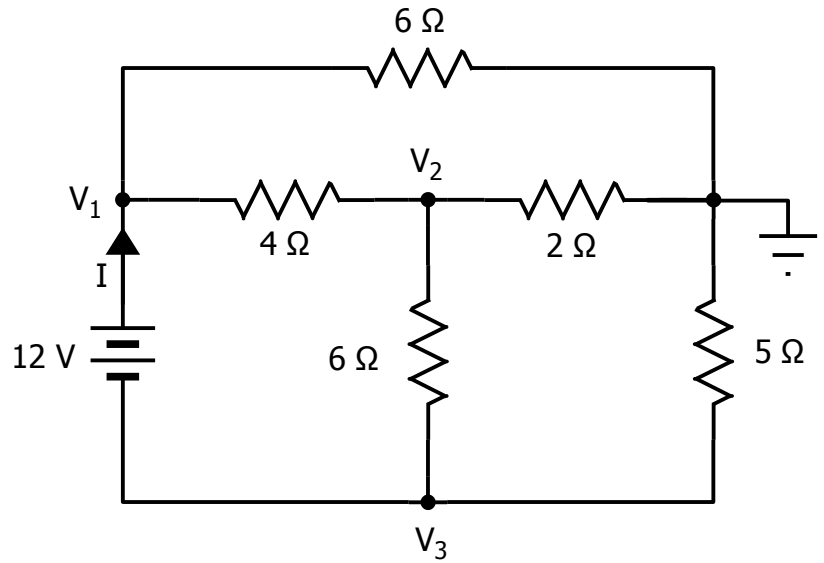(Note: with the ground at a different node, you now have 3 unknown nodes. But you also know the voltage relationship between 2 of them.)



$$V_1 - V_3 = 12$$

$$\frac{V_2 - V_1}{4} + \frac{V_2 - V_3}{6} + \frac{V_2}{2} = 0$$

$$\frac{V_1 - V_2}{4} + \frac{V_1}{6} - I = 0$$

$$\frac{V_3 - V_2}{6} + \frac{V_3}{5} + I = 0$$

$$3V_2 - 3V_1 + 2V_2 - 2V_3 + 6V_2 = 0$$

$$3V_1 - 3V_2 + 2V_1 - 12I = 0$$

$$5V_3 - 5V_2 + 6V_3 + 30I = 0$$

$$\begin{bmatrix} 1 & 0 & -1 & 0 \\ -3 & 11 & -2 & 0 \\ 5 & -3 & 0 & -12 \\ 0 & -5 & 11 & 30 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \\ I \end{bmatrix} = \begin{bmatrix} 12 \\ 0 \\ 0 \\ 0 \end{bmatrix}$$

$$V_1 = 5.88 \text{ V}$$

$$V_2 = 0.49 \text{ V}$$


$$V_3 = -6.12 \text{ V}$$

$$I = 2.33 \text{ A}$$

ECE3 Fall 2020

Practice Problems 2

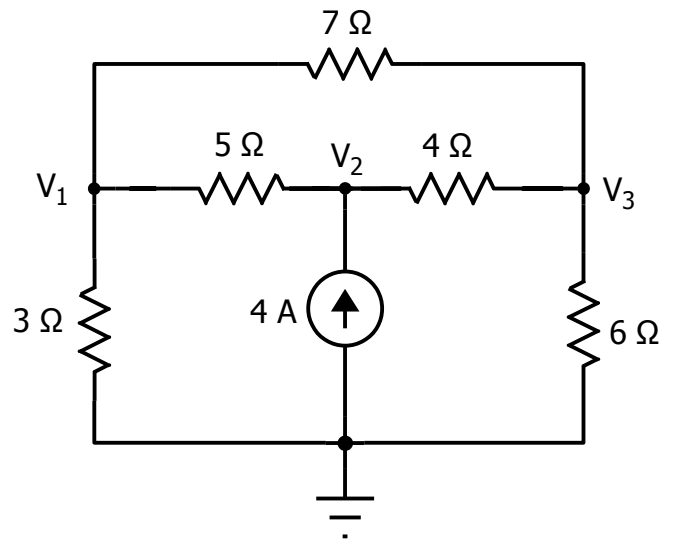4. Find the three voltages. You may need to dig a little to work this problem.



$$\frac{V_1 - V_2}{5} + \frac{V_1}{3} + \frac{V_1 - V_3}{7} = 0$$

$$\frac{V_2 - V_1}{5} - 4 + \frac{V_2 - V_3}{4} = 0$$

$$\frac{V_3 - V_1}{7} + \frac{V_3 - V_2}{4} + \frac{V_3}{6} = 0$$

$$21V_1 - 21V_2 + 35V_1 + 15V_1 - 15V_3 = 0$$

$$4V_2 - 4V_1 - 80 + 5V_2 - 5V_3 = 0$$

$$24V_3 - 24V_1 + 42V_3 - 42V_2 + 28V_3 = 0$$

$$71V_1 - 21V_2 - 15V_3 = 0$$

$$-4V_1 + 9V_2 - 5V_3 = 80$$

$$-24V_1 - 42V_2 + 94V_3 = 0$$

$$V_1 = 7.2 \text{ V}$$

$$V_2 = 17.4 \text{ V}$$


$$V_3 = 9.6 \text{ V}$$

ECE3 Fall 2020

Practice Problems 2

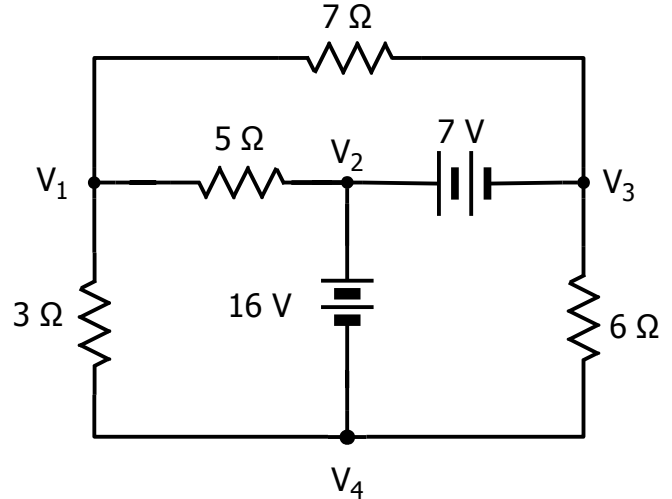5. Choose (judiciously) a reference node. Then find the current through the 7 V battery.

You may need to dig a little to work this problem. Note: if you choose to solve this problem using Mesh Current Analysis, you are on your own.



CHOOSING V_4 TO BE THE REFERENCE NODE,

$V_2 = 16$ V, and $V_3 = 9$ V

$$\frac{V_1 - 16}{5} + \frac{V_1}{3} + \frac{V_1 - 9}{7} = 0$$

$$21V_1 - (16)(21) + 35V_1 + 15V_1 - 135 = 0$$

$$71V_1 = 471$$

$$V_1 = 6.6$$
 V

KCL at the right end of the 7 V battery (currents assumed to be leaving unless known otherwise):

$$\frac{V_3 - 0}{6} + \frac{V_3 - V_1}{7} + I_7 = 0$$

$$1.50 + 0.34 + I_7 = 0$$

$$I_7 = -1.84$$
 A (left to right, into the node)

CHOOSING V_2 TO BE THE REFERENCE NODE,

$V_4 = -16$ V, and $V_3 = -7$ V

$$\frac{V_1 + 16}{3} + \frac{V_1}{5} + \frac{V_1 + 7}{7} = 0$$

$$35V_1 + (16)(35) + 21V_1 + 15V_1 + 105 = 0$$

$$71V_1 = -665$$

$$V_1 = -9.4$$
 V

KCL at the right end of the 7 V battery (currents assumed to be leaving unless known otherwise):

$$\frac{V_3 - V_4}{6} + \frac{V_3 - V_1}{7} + I_7 = 0$$

$$1.50 + 0.34 + I_7 = 0$$

$$\frac{-7 - (-16)}{6} + \frac{-7 - (-9.4)}{7} + I_7 = 0$$

$$1.50 + 0.34 + I_7 = 0$$

$$I_7 = -1.84$$
 A (left to right, into the node)


ECE3 Fall 2020

Practice Problems 2

These problems will exercise your knowledge of KVL and KCL. Be sure to watch the video. "Legal" means that KCL and KVL are satisfied.


4. Is this a "legal" circuit? If not, why not?

Circuit is legal.

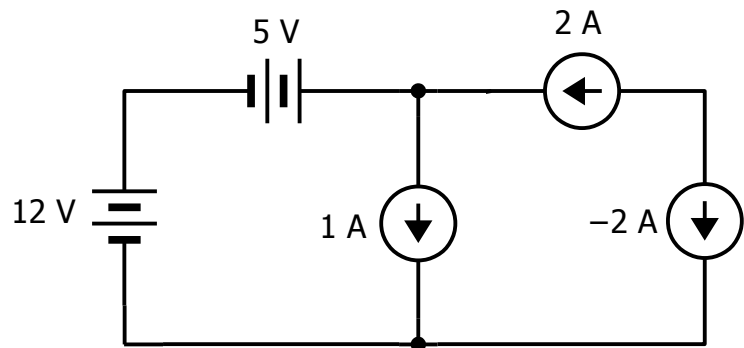

5. Is this a "legal" circuit? If not, why not?

Circuit is illegal.

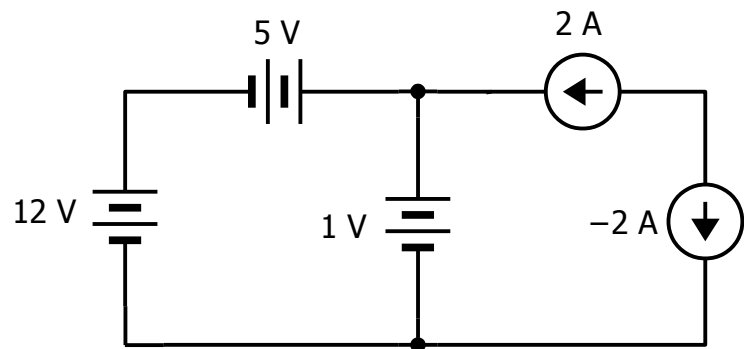

ECE3 Fall 2020

Practice Problems 2