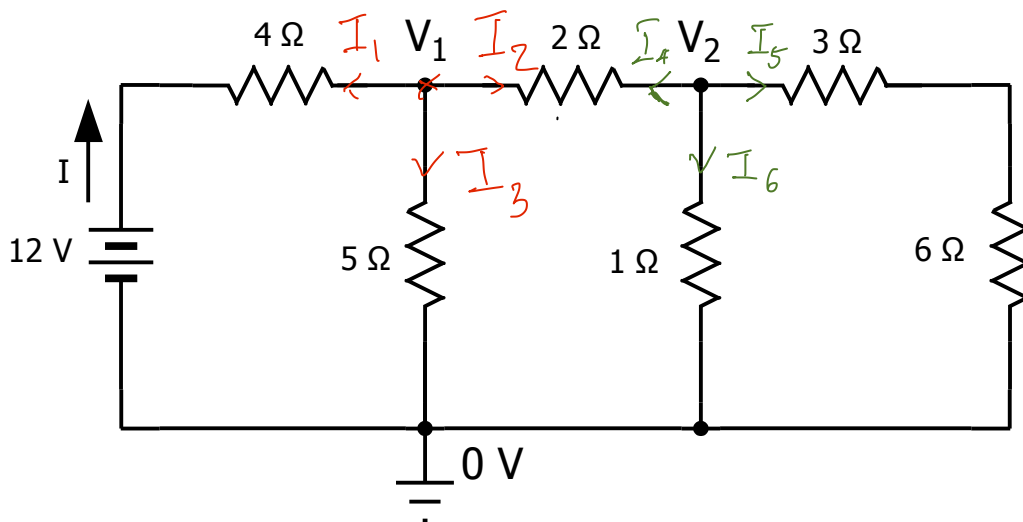


EE3 Fall 2018
Practice Problems 2

What Ho
105 355311



1. Watch and study the KVL-KCL video as posted under Week 1.
 - a. Assuming that all of the currents at Node 1 (where V_1 is) are *leaving* the node, write an Ohm's Law expression for the current going through the 4Ω resistor.
 - b. Under the same assumption, write an Ohm's Law expression for the current through the 5Ω resistor.
 - c. Continuing, write an expression for the current through the 2Ω resistor.
 - d. Now, combine the answers to 1a,b,c into a KCL equation.
 - e. Now, following the procedures in a, b, and c, write Ohm's Law expressions for the three currents leaving Node 2.
 - f. Combine the three answers to 1e into a second KCL equation.
2. You now have 2 equations in 2 unknowns. Solve them for V_1 and V_2 .
3. Now that you know V_1 , you can compute I .

$$a) \frac{V_1 - 12V}{4\Omega} = I_1 \quad b) I_3 = \frac{V_1}{5\Omega}$$

$$c) I_2 = \frac{V_1 - V_2}{2\Omega}$$

$$d) \text{ we have: } I_1 + I_2 + I_3 = 0$$

$$\Rightarrow \frac{V_1 - 12}{4} + \frac{V_1}{5} + \frac{V_1 - V_2}{2} = 0$$

$$\Rightarrow \frac{5(V_1 - 12) + 4V_1 + 10(V_1 - V_2)}{20} = 0$$

$$\Leftrightarrow 5V_1 - 60 + 4V_1 + 10V_1 - 10V_2 = 0$$

$$\Leftrightarrow \boxed{19V_1 - 10V_2 = 60} \quad (1)$$

$$e) \quad I_4 = \frac{V_2 - V_1}{2\Omega} \quad ; \quad I_5 = \frac{V_2}{3\Omega + 6\Omega} = \frac{V_2}{9\Omega}$$

$$I_6 = \frac{V_2}{1\Omega} \quad , \quad \text{Also } I_4 + I_5 + I_6 = 0 \quad (\text{KCL})$$

$$\Rightarrow \frac{V_2 - V_1}{2} + \frac{V_2}{9} + \frac{V_2}{1} = 0$$

$$\Leftrightarrow \frac{9(V_2 - V_1) + 2V_2 + 18V_2}{18} = 0$$

$$\Leftrightarrow 9V_2 - 9V_1 + 2V_2 + 18V_2 = 0$$

$$\Leftrightarrow -9V_1 + 29V_2 = 0 \quad \Leftrightarrow \boxed{9V_1 - 29V_2 = 0} \quad (2)$$

f) Combine with (1), we have:

$$\begin{cases} 19V_1 - 10V_2 = 60 & (1) \\ 9V_1 - 29V_2 = 0 & (2) \end{cases}$$

2) Solve these equations

From (2), $V_1 = \frac{29V_2}{9}$, plug it into (1), we have

$$19 \times \frac{29V_2}{9} - 10V_2 = 60$$

$$\Rightarrow \frac{461}{9} V_2 = 60 \Rightarrow \boxed{V_2 = 1.17(V)}$$

$$\Rightarrow \boxed{V_1 = \frac{29V_2}{9} = 3.774(V)}$$

3) From 1a, we have:

$$\frac{V_1 - 12V}{4\Omega} = I_1 \Rightarrow I_1 = \frac{3.774 - 12}{4\Omega}$$

$$\Rightarrow \boxed{I_1 = -2.06(A)}$$

Also, following the circuit $I = -I_1$

$$\Rightarrow \boxed{I = 2.06(A)}$$