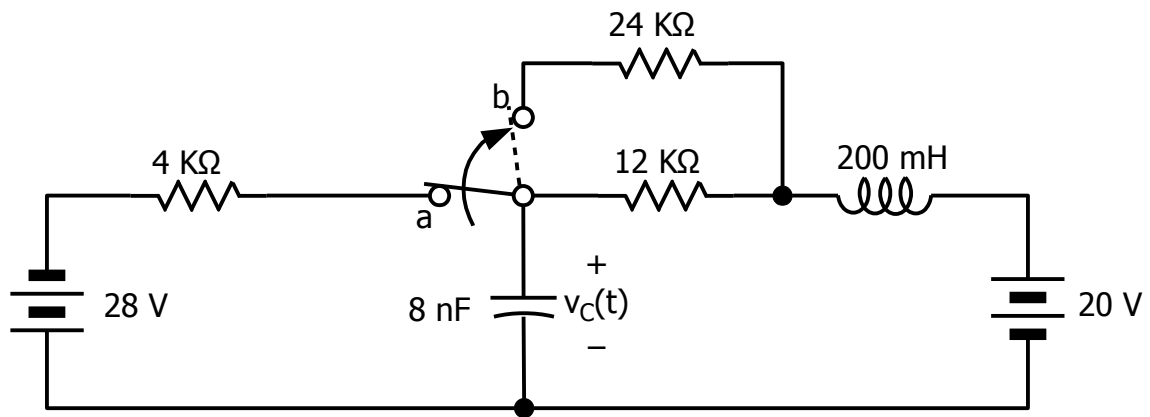


# EE3 Fall 2020

## Practice Problems 4



1. The switch has been in position a for a long time. All transients have died out. At  $t = 0$ , the switch moves instantaneously to position b.
  - a. At  $t=0^-$  (the last instant that the switch is in position a), what is the current through the capacitor? 0 A
  - b. At  $t=0^-$  (the last instant that the switch is in position a), what is the voltage across the capacitor?  $-28 - v_C(0^-) + (4K\Omega)(3mA) = 0$ ;  $v_C(0^-) = -16 V$
  - c. At  $t=0^+$  (the first instant that the switch is in position b), the current through the capacitor is the same as in Part a.    True False
  - d. At  $t=0^+$  (the first instant that the switch is in position b), the voltage across the inductor is the same as at  $t=0^-$ .    True False
  - e. At  $t=0^+$  (the first instant that the switch is in position b), what is the voltage across the inductor?
 


$KVL\ CCW: -20 + v_L(0^+) + (8K\Omega)(3mA) + v_C(0^+) = 0$ ;  $v_L(0^+) = 12 V$ ; + at right end

## EE3 Fall 2020

### Practice Problems 4

2. This is a second-order circuit. There is an initial voltage on the capacitor  $v(0^-) = 12$  V, and an initial current in the inductor  $i_L(0^-) = 30$  mA. In order to solve the differential equation for  $v(t)$ , the following values must be found:

- $i_C(0^+)$
- $i_R(0^+)$
- $dv(t)/dt|_{t=0^+}$

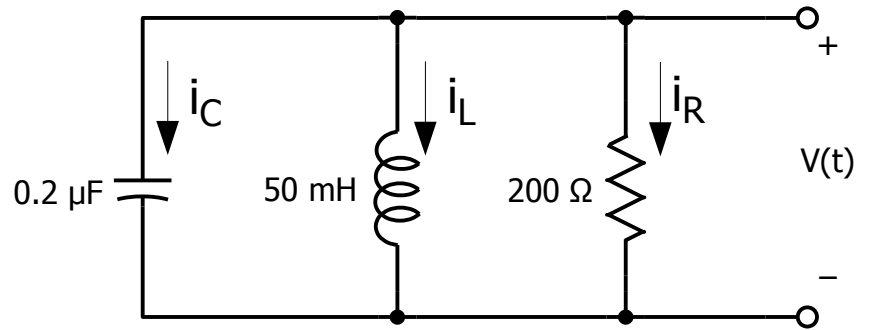

Using what you know about inductors, capacitors, and KCL, find these values.

$$i_L(0^+) = i_L(0^-) = 30 \text{ mA}$$

$$v(0^+) = v(0^-) = 12 \text{ V}$$

$$\text{a. } i_C(0^+) + i_L(0^+) + i_R(0^+) = 0$$

$$i_C(0^+) = (-30 - 60) = -90 \text{ mA}$$

$$\text{b. } i_R(0^+) = \frac{v(0^+)}{R} = \frac{12}{200} = 60 \text{ mA}$$


$$\text{c. Because } i_C(0^+) = C \left. \frac{dv(t)}{dt} \right|_{t=0^+}$$

$$\left. \frac{dv(t)}{dt} \right|_{t=0^+} = \frac{-90 \text{e-}3}{0.2 \text{e-}6} = -450 \text{ KV/s}$$

## EE3 Fall 2020
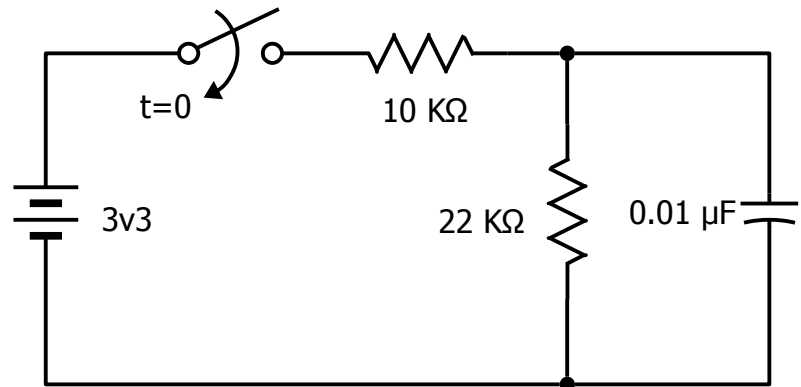
### Practice Problems 4

- 3a. Find the time constant  $\tau$  of this circuit. This will require solving the differential equation for the circuit.
- 3b. Then, find only the Thévenin resistance  $R_{th}$  of the circuit to the left of the capacitor (consider the capacitor to be the load).
- 3c. Then, compute  $R_{th} \cdot C$  and compare to the  $\tau$  from 3a.



$$\frac{v_C - 3.3}{10e3} + \frac{v_C}{22e3} + 1e-8 \frac{dv_C}{dt} = 0$$

$$\frac{dv_C}{dt} + (1e8) \left( \frac{1}{10e3} + \frac{1}{22e3} \right) v_C = (1e8) \left( \frac{3.3}{10e3} \right)$$

$$P = 1.45e4; Q = 3.3e4; e^{\int_0^t P dx} = e^{1.45e4 t}$$

$$e^{1.45e4 t} \frac{dv_C}{dt} + 1.45e4 e^{1.45e4 t} v_C = 3.3e4 e^{1.45e4 t}$$

$$\frac{d}{dt} (e^{1.45e4 t} v_C) = 3.3e4 e^{1.45e4 t}$$

$$e^{1.45e4 t} v_C = \int 3.3e4 e^{1.45e4 t} dt = \frac{3.3e4}{1.45e4} e^{1.45e4 t} + C = 2.27 e^{1.45e4 t} + C$$

$$v_C = 2.27 + C e^{-1.45e4 t}$$

$$v_C(0^+) = 2.27 + C \rightarrow C = -2.27$$

$$v_C(t) = 2.27(1 - e^{-1.45e4 t})$$

$$\text{Time constant } \tau = \frac{1}{1.45e4} = 6.875e-5 \text{ s}$$

$R_{th}$  of network assuming C is the load:

$$R_{th} = 10e3 || 22e3 = 6.875e3 \Omega$$

$$R_{th} \cdot C = (6.875e3)(1e-8) = 6.875e-5 \text{ s}$$

CONCLUSION: for a first-order capacitive circuit with step input,  $\tau = \frac{1}{P}$  !

Also,  $\tau = C \cdot R_{th}$ , where C is the load! NOTE: not a mathematical proof.

## EE3 Fall 2020 Practice Problems 4

4. The switch has been in the position shown for a long time. Find:

a.  $i_L(0^+)$


b.  $i_O(0^+)$

c.  $v_O(0^+)$

d.  $\tau$  for  $t=0^+$

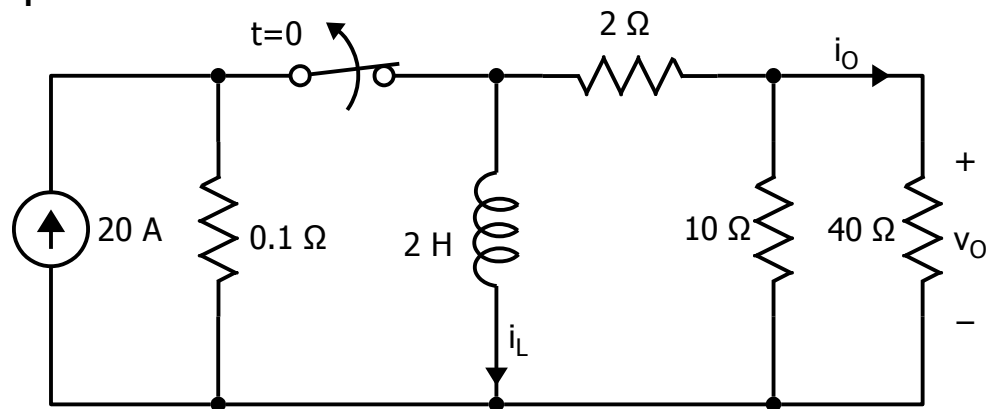e.  $i_L(0^+)$  for all  $t>0$

(HINT: refer to the Lecture 4 video at 22 minutes.)



a.  $i_L(0^+) = i_L(0^-) = 20 \text{ A}$

b.  $i_O(0^+) = -20 \left( \frac{10}{10+40} \right) = -4 \text{ A}$

c.  $v_O(0^+) = (-4) \cdot (40) = -160 \text{ V}$

d.  $\tau = \frac{L}{R_{th}}$

$$R_{th} = 2 + 10 \parallel 40 = 2 + 8 = 10 \Omega$$

$$\tau = \frac{2}{10} = 0.2 \text{ s}$$

e. Refer to the Lecture 4 video at 22 minutes.


$$i_L(t) = i_O(0^+) e^{\frac{-t}{\tau}} = 20 e^{-5t}$$

# EE3 Fall 2020

## Practice Problems 4

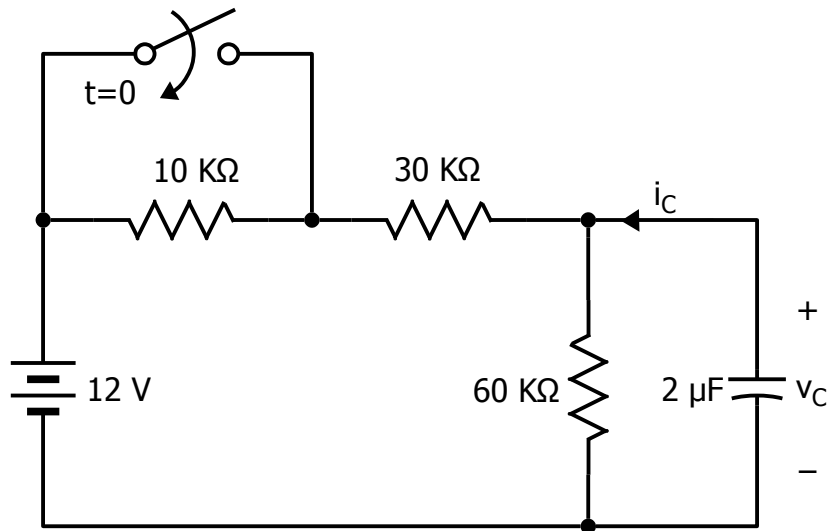5. The switch has been open for a long time. Find:

- $v_C(0^-)$
- $v_C(0^+)$
- $v_C(\infty)$
- $i_C(0^-)$
- $i_C(0^+)$



$$\text{a. } v_C(0^-) = 12 \left( \frac{60}{60+40} \right) = 7.2 \text{ V}$$

$$\text{b. } v_C(0^+) = v_C(0^-) = 7.2 \text{ V}$$

$$\text{c. } v_C(\infty) = 12 \left( \frac{60}{60+30} \right) = 8 \text{ V}$$

$$\text{d. } i_C(0^-) = 0$$

$$\text{e. } \frac{7.2-12}{30\text{e}3} + \frac{7.2}{60\text{e}3} - i_C(0^+) = 0$$

$$i_C(0^+) = \frac{21.6-24}{60\text{e}3} = 0.04 \text{ mA}$$