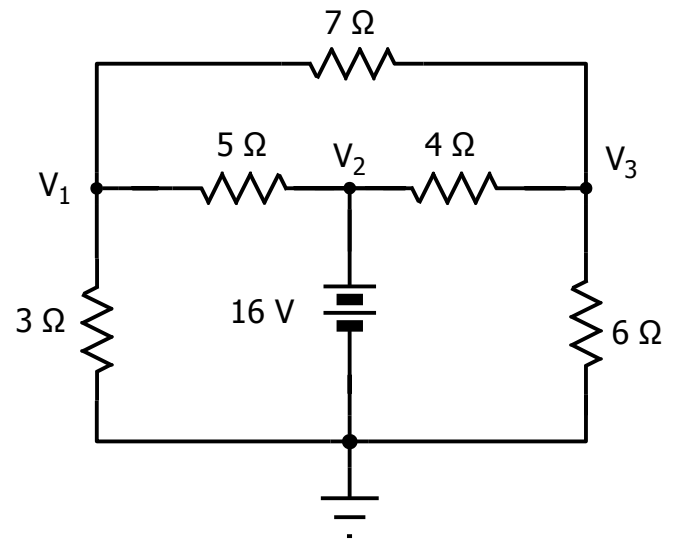


# EE3 Fall 2020

## Practice Problems 5

1. More NVA practice. Find  $V_1$  &  $V_3$ .



$$\frac{V_1 - 16}{5} + \frac{V_1}{3} + \frac{V_1 - V_3}{7} = 0$$

$$\frac{V_3 - V_1}{7} + \frac{V_3 - 16}{4} + \frac{V_3}{6} = 0$$

$$71V_1 - 15V_3 = 336$$


$$-24V_1 + 94V_3 = 672$$

$$V_1 = 6.6 \text{ V}; V_3 = 8.83 \text{ V}$$

## EE3 Fall 2020 Practice Problems 5

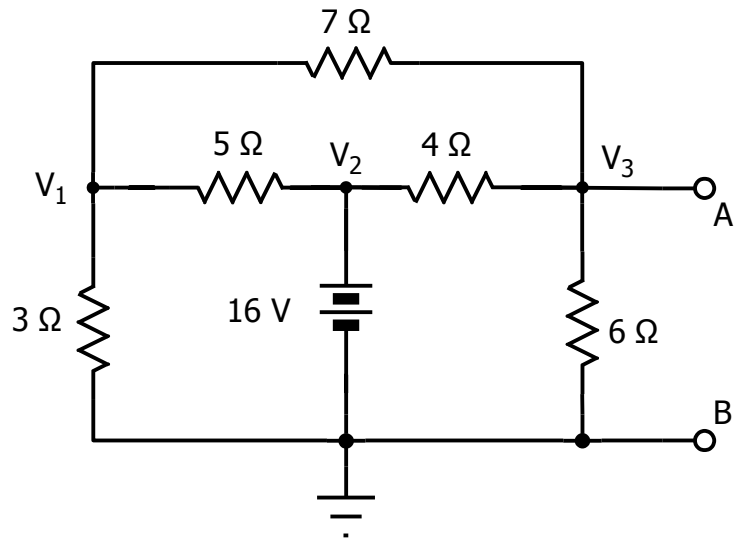2. In this circuit,  $V_3 = 8.8 \text{ V}$ . You will be using Method (a.) to find the Thévenin Equivalent circuit.

Use the  $V_{OC}$ - $I_{SC}$  method to find the Thévenin Equivalent circuit, looking in through Port A-B.



From Problem 1,  $V_3 = 8.8 \text{ V}$

$$V_{OC} = V_3 = 8.8 \text{ V}$$

Shorting Terminals A and B,

$$\frac{V_1 - 16}{5} + \frac{V_1}{3} + \frac{V_1}{7} = 0$$

$$\frac{0 - 16}{4} + \frac{0 - V_1}{7} + I_{SC} = 0$$

$$V_1 = \frac{336}{71} = 4.7324$$

$$I_{SC} = \frac{V_1 + 112}{28} = 4.6761$$


$$R_{th} = \frac{V_{OC}}{I_{SC}} = \frac{8.8}{4.6761} = 1.88 \text{ } \Omega$$

NOTE: This problem shows Method (a.) to finding the Thévenin Equivalent circuit.

## EE3 Fall 2020

### Practice Problems 5

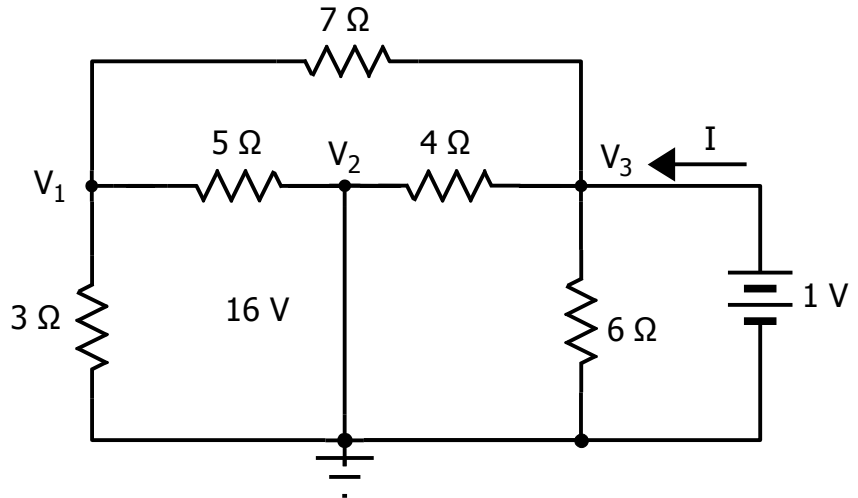3. This time, you will find the Thévenin Equivalent circuit by using Method (b.). We zeroed out the 16 V battery and attached a test battery to the circuit as shown.
- Find an expression for the current  $I_T$ .
  - Compute  $V_T / I_T$ . Units are ohms.
  - Compare your answer to Problem 2.




$$\begin{aligned}
 V_2 &= 0 \text{ V}; V_3 = 1 \text{ V} \\
 \frac{V_1 - 0}{3} + \frac{V_1 - 0}{5} + \frac{V_1 - 1}{7} &= 0 \\
 V_1 &= \frac{15}{71} = 0.2113 \text{ V} \\
 -I + \frac{1 - 0 \text{ V}}{4 \Omega} + \frac{1 \text{ V}}{6 \Omega} + \frac{1 - 0.2113 \text{ V}}{7 \Omega} &= 0 \\
 I &= 0.53 \text{ A} \\
 \frac{1 \text{ V}}{I} &= \frac{1}{0.53} = 1.89 \Omega
 \end{aligned}$$

## EE3 Fall 2020

### Practice Problems 5

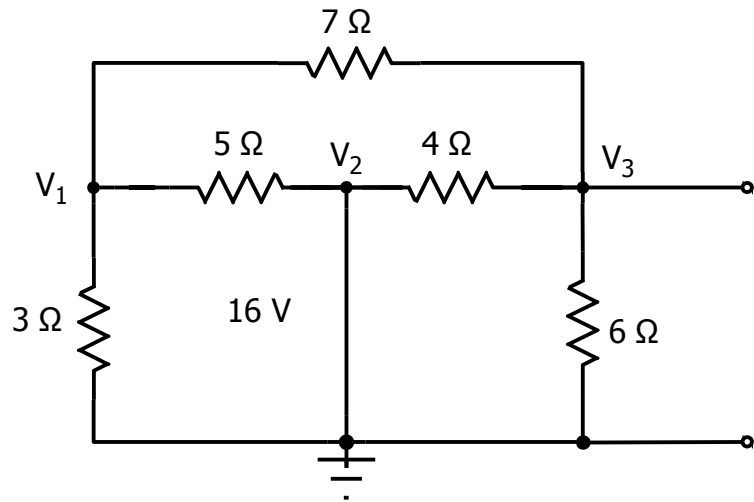
4. This time, you will find the Thévenin Equivalent circuit by using Method (c.). We replaced the 16 V battery with a short.
- Using your knowledge of series and parallel circuits, find the resistance of the circuit when looking in through the port.
  - Compare your answer to Problem 3.



$$(7+5||3) \parallel (4||6) = 1.89 \, \Omega$$
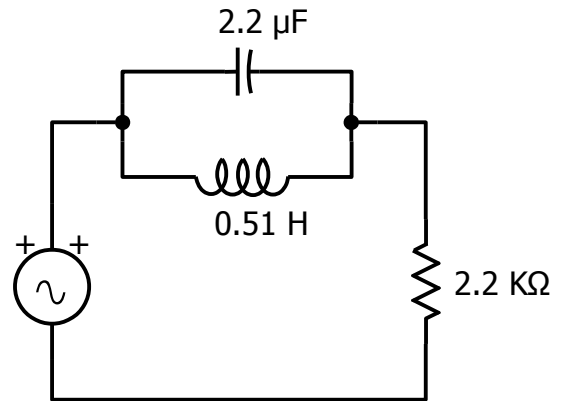
## EE3 Fall 2020 Practice Problems 5

- 5a. Using the expressions for capacitive and inductive impedance, find the total impedance presented by the capacitor, inductor, and resistor to the voltage source. Set  $\omega = 1000$  rad/s.



$$Z_{tot} = Z_C \parallel Z_L + R$$

$$Z_C \parallel Z_L + R = \frac{Z_C Z_L}{Z_C + Z_L} + R = \frac{\frac{j\omega L}{j\omega C} + R}{\frac{1}{j\omega C} + j\omega L} = \frac{\frac{j 1000 \cdot 0.51}{j 1000 \cdot 2.2 \text{e-}6} + 2200}{\frac{1}{j 1000 \cdot 2.2 \text{e-}6} + j 1000 \cdot 0.51}$$

$$Z_{tot} = 2200 - j 4180$$

- b. Now find the current through the voltage source if  $v(t) = 10 \cos(1000t)$ . Express in both rectangular and polar forms.

$$i_V(t) = \frac{v(t)}{Z_{tot}} = \frac{10 \angle 0^\circ}{2200 - j 4180} = 0.99 + j 1.87 \text{ mA} = 2.12 \angle 62.1^\circ$$

- d. Find the current through the inductor  $i_L$ . Express in both rectangular and polar forms.

$$i_L(t) = i_V(t) \left( \frac{Z_C}{Z_C + Z_L} \right) = (0.99 + j 1.87) \left( \frac{-j 454}{-j 454 + j 510} \right) = -8.1 - j 15.4 \text{ mA} = 17.4 \angle -118^\circ$$

- e. Find the current through the capacitor  $i_C$ .

$$i_C(t) = i_V(t) \left( \frac{Z_L}{Z_L + Z_C} \right) = (0.99 + j 1.87) \left( \frac{j 510}{-j 454 + j 510} \right) = 9.1 + j 17.2 \text{ mA} = 19.5 \angle 62.1^\circ$$

- f. Add  $i_L$  and  $i_C$ . The sum should equal the current in #2.

$$i_L + i_C = -8.1 - j 15.4 + 9.1 + j 17.2 = 0.99 + j 1.87 \text{ mA}$$

- g. Compare the magnitudes of  $i_L(t)$ ,  $i_C(t)$ , and  $i_V(t)$ . Can you explain the apparent anomaly?

NOTE:  $|i_L(t)|$  and  $|i_C(t)|$  are much larger than  $|i_V(t)|$ !