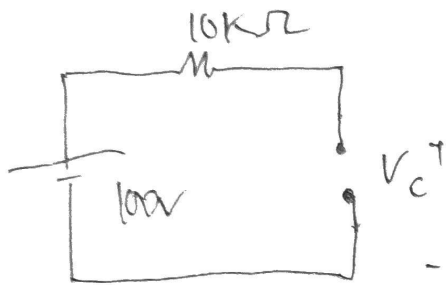


Nhat Ho


105355311

The Switch has been in position ①
for a long time, we have

a circuit which the capacitor
is open circuit to DC, so.




$$\rightarrow V_c(0^-) = 100V$$

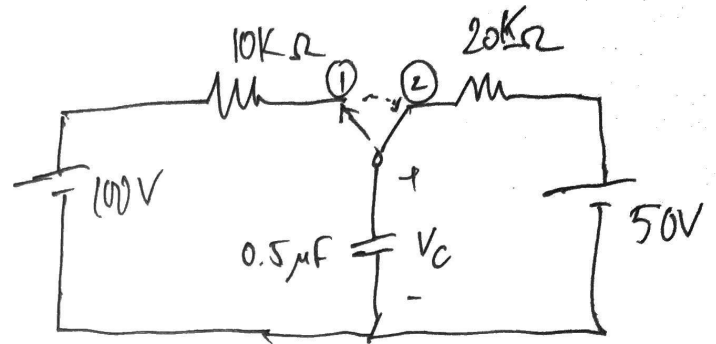

When Switch move to position ②.


at $t \rightarrow 0^+$, we have $V_c(0^-) = V_c(0^+) = 100(V)$

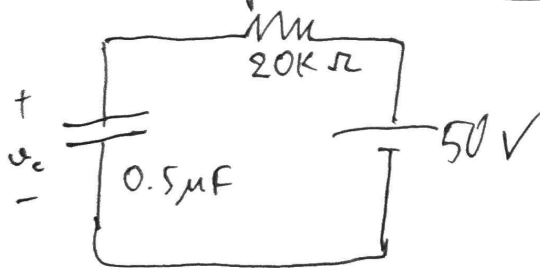Because the capacitor will not allow instantaneous change
in voltage. And we have:



$$\tau = RC = 20 \times 10^3 \times 0.5 \times 10^{-6} = 0.01 (\text{sec})$$

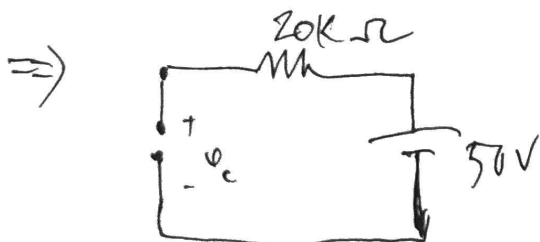Since the capacitor acts like an
open circuit to DC for a long time



$$\Rightarrow \boxed{V_c = 50V}$$