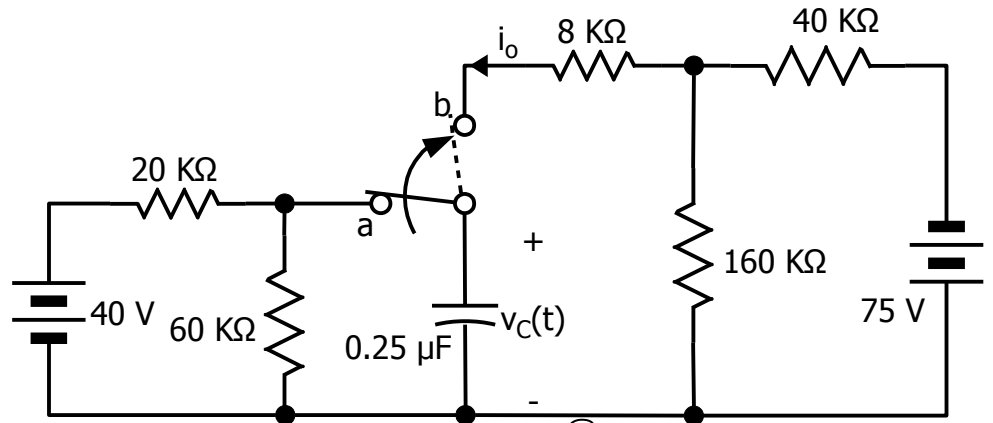


EE3 Fall 2020 Homework Problem 3


What Ho
105355311

The switch has been in position a for a long time. At $t=0$, it moves instantaneously to position b. Find:

- $v_c(0^-)$
- $v_c(0^+)$
- $i_o(0^-)$
- $i_o(0^+)$
- [EXTRA CREDIT] $v_c(t)$



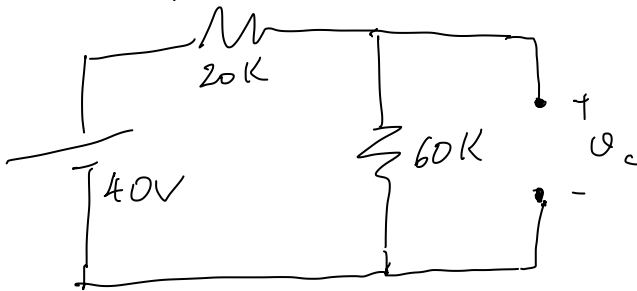a) When switch states at a for a long time, the capacitor is open circuit to DC, we have:



$$\Rightarrow v_c = \frac{60k}{60k + 20k} \times 40 = 30 (V)$$


$$\Rightarrow v_c(0^-) = 30 (V)$$

b) At $t=0$, the switch move instantaneously to position b. We have: $v_c(0^+) = v_c(0^-) = 30(V)$. Because the capacitors will not allow instantaneous change in voltage.

c) at $t=0^-$, $i_o = 0$. Because at $t=0^-$, the circuit is opened, and no current through the $8k\Omega$ resistor.

d) at $t=0^+$, we have known already $v_c(0^+) = 30V$. And we can have a new circuit:

What Ho
105 355 311

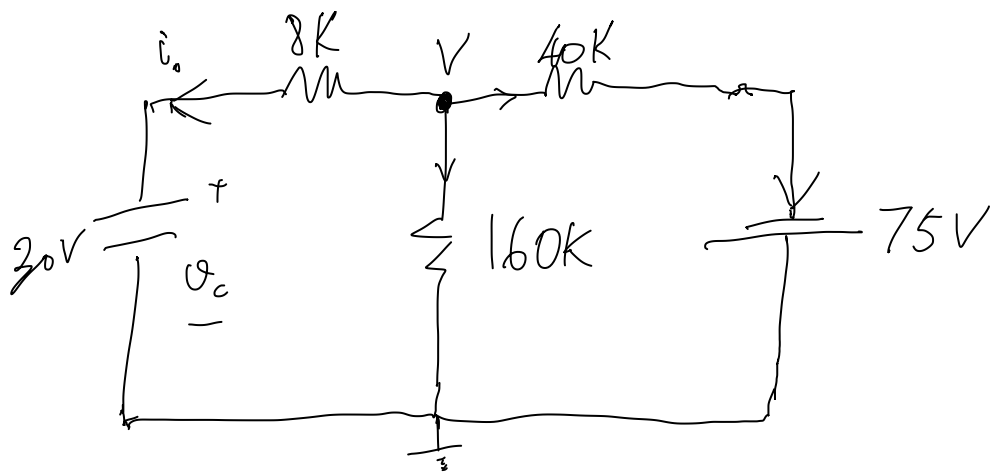

We have

$$\frac{V - 30}{8K} + \frac{V}{160K} + \frac{V + 75}{40K} = 0$$


$$\Rightarrow 20(V - 30) + V + 4(V + 75) = 0$$

$$\Rightarrow 25V = 300 \Rightarrow V = 12 \text{ (V)}$$

$$\Rightarrow i_o = \frac{V - 30}{8K} = \frac{12 - 30}{8K} = \frac{-18V}{8K} = -2.25 \text{ (mA)}$$

$$\Rightarrow i_o(0^+) = -2.25 \text{ (mA)}$$

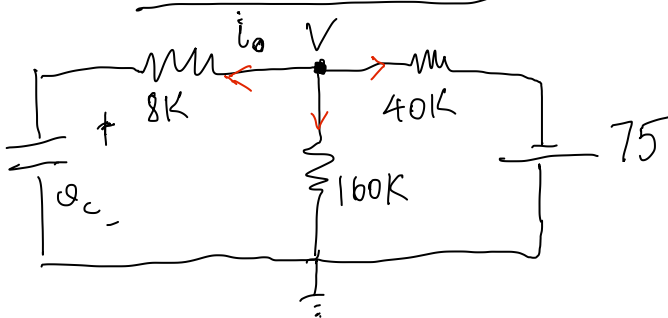e) Find $V_c(t)$ We have at $t = 0^+$, $\vartheta_c(0^+) = 30V$



$$\frac{V - \vartheta_c}{8K} + \frac{V}{160K} + \frac{V + 75V}{40K} = 0$$

$$\frac{V - \vartheta_c}{8K} = i_o \Rightarrow V = 8K i_o + \vartheta_c$$

$$\Rightarrow i_o + \frac{8K i_o + \vartheta_c}{160K} + \frac{8K i_o + \vartheta_c + 75V}{40K} = 0$$

$$\Rightarrow 160K.i_0 + 8K.i_0 + v_c + 4.(8K.i_0 + v_c + 75V)$$

$$= 168K.i_0 + v_c + 32K.i_0 + 4v_c + 300V = 0$$

$$= 200K.i_0 + 5v_c + 300V = 0$$

$$= 40K.i_0 + v_c + 60V = 0 \quad \text{Beside } i_0 = i_c = C \frac{dv_c}{dt}$$

$$\Rightarrow 40K.C \frac{dv_c}{dt} + v_c + 60V = 0$$

$$\Rightarrow 40K.C \frac{dv_c}{dt} = -(v_c + 60V)$$

$$\Rightarrow \frac{dv_c}{v_c + 60V} = \frac{-dt}{40K.C} \Rightarrow \int_{v_c(0^+)}^{v_c(t)} \frac{dv_c}{v_c + 60V} = \int_{t=0^+}^t \frac{-dt}{40K.C}$$

$$\text{Also, } v_c(0^+) = 30V.$$

$$\Rightarrow \ln(v_c + 60V) \Big|_{30V}^{v_c(t)} = \frac{-t}{40K.C}$$

$$\Rightarrow \frac{v_c(t) + 60V}{90V} = e^{-t/40K.C}$$

$$\Rightarrow v_c(t) = -60V + 90V \cdot e^{-t/40K.C}$$

We have: $\tau = 40K.C = 40 \times 10^3 \times 0.25 \times 10^{-6} = 0.01$

$$\Rightarrow v_c(t) = -60V + 90V e^{-t/0.01}$$

$$\Rightarrow \boxed{v_c(t) = -60V + 90V e^{-100t} \quad (V)}$$

What Ho
105355311