

EE3 Fall 2020

Practice Problems 7

1. Compute the forward resistance of the 1N4448 diode when working in the normal operating range of 4-20 mA.


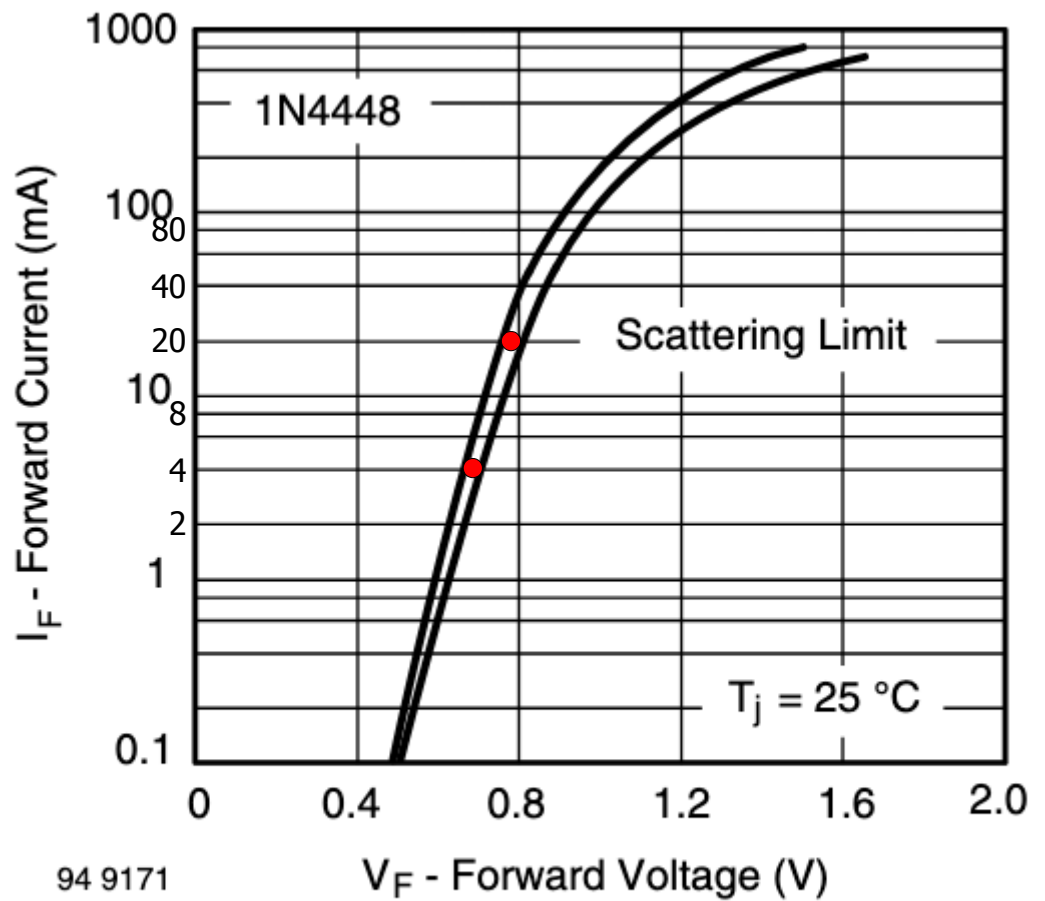


Fig. 2 - Forward Current vs. Forward Voltage

$$R = 6.25\ \Omega$$

EE3 Fall 2020 Practice Problems 7

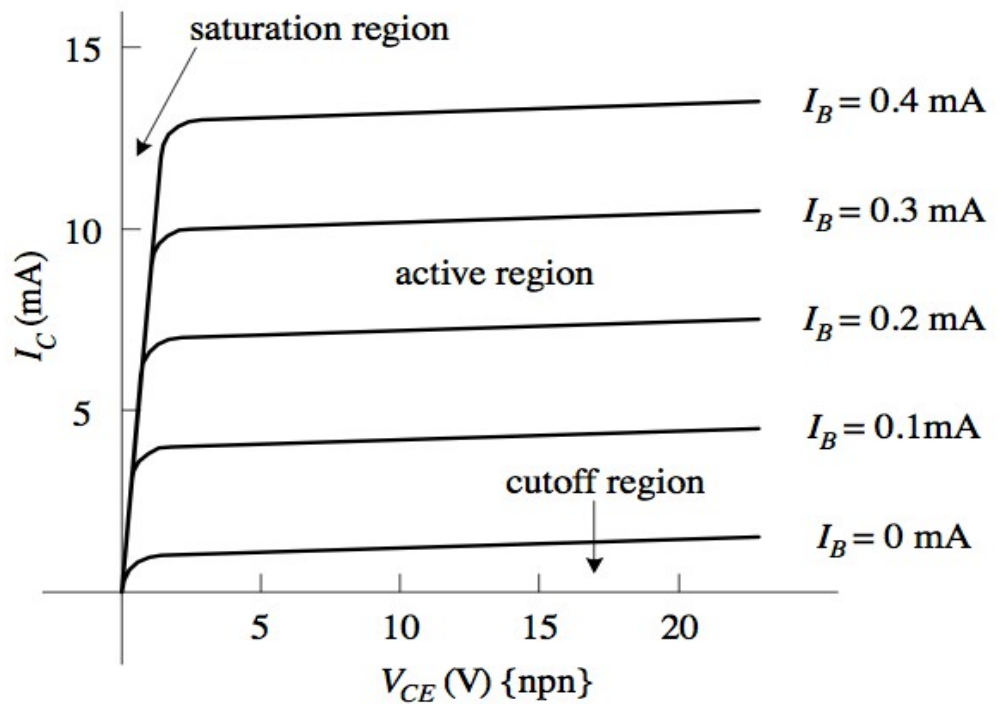
2. Compute the approximate current gain of this NPN transistor if the input base current is ± 0.1 mA with an offset of 0.2 mA. Current gain $G = I_C/I_B$.



$$G = 30 \text{ (rather low for a BJT)}$$

EE3 Fall 2020 Practice Problems 7

One can make use of resonance to provide amplification at a given frequency. In this circuit, we want the gain $|V_{\text{out}}/V_{\text{in}}|$ to be 10 at 1 KHz. Find L and C.

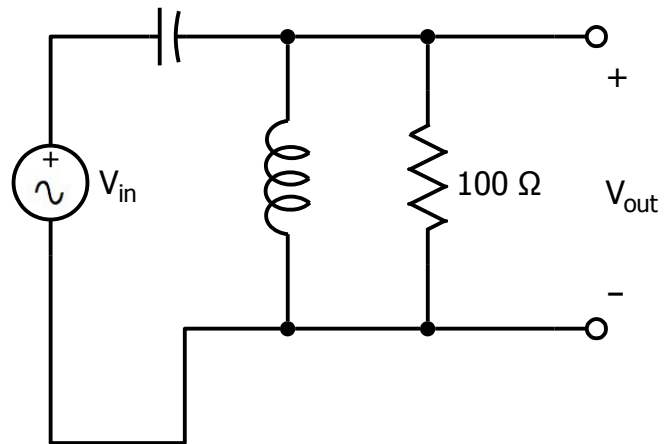

$$C = 15.9\ \mu\text{F}$$
$$L = 1.59\ \text{mH}$$