

ECE3 Fall 2020

Quiz 1

Name _____ | _____
Family (Last) Name Given (First) Name

- a. Find the resonant frequency f_0 of this circuit IN HERTZ.
NOTE: pF is picofarads (10^{-12} F).
- b. What type of filter is this?
- Low Pass
 - High Pass
 - Band Pass
 - Band Reject

