Qui7 8:

because: 
$$i = \frac{V}{Z_1} = \frac{1020^{\circ}(V)}{j20(\Omega)} = \frac{1020^{\circ}}{2020^{\circ}} = \frac{10}{20}20^{\circ}$$