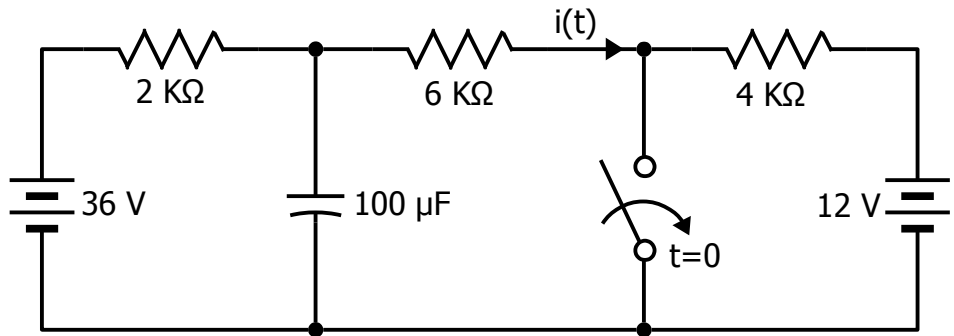


EE3 Fall 2020
Homework Problem 7

What Ho
105 355 311

This problem is all about $i(t)$.


- What is $i(0^-)$?
- What is $i(0^+)$?
- What is $i(\infty)$?
- What is $i(t)$, $t > 0$?



The circuit has been in this condition for a long time.

This problem can be solved without using a differential equation, though you may do so this way if you wish. Solving it without using a differential equation is done by pulling together a few ideas and bringing them to bear on the problem. That means using the answers to the first 3 parts of this problem, plus the judicious use of a Thévenin equivalent, plus the third slide of Lecture 4 in Week 4 of CCLE.

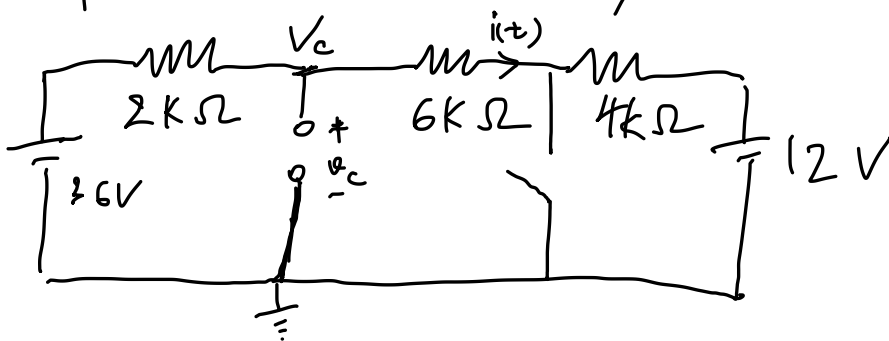1) When the switch opens for a long time, the capacitor is opened circuit to DC, we have:



$$\Rightarrow -36 + i(2k\Omega + 6k\Omega + 4k\Omega) + 12 = 0 \text{ (KVL)}$$

$$\Rightarrow 12k\Omega i = 36 - 12 = 24 \text{ (V)}$$

$$\Rightarrow i = i(0^-) = \frac{24 \text{ V}}{12000 \Omega} = \boxed{0.002 \text{ (A)} = 2 \text{ (mA)}}$$


We also have: $-36 + i \cdot 2k\Omega + V_c = 0$

$$\Rightarrow V_c = V_c(0^-) = 36 - 0.002 \text{ A} \times 2000 \Omega = 32 \text{ (V)}$$

b) At $t = 0^+$, the switch closes

$\Rightarrow V_c(0^-) = V_c(0^+) = 32 \text{ V}$ because the capacitor will not allow instantaneous change in voltage.

We also have:

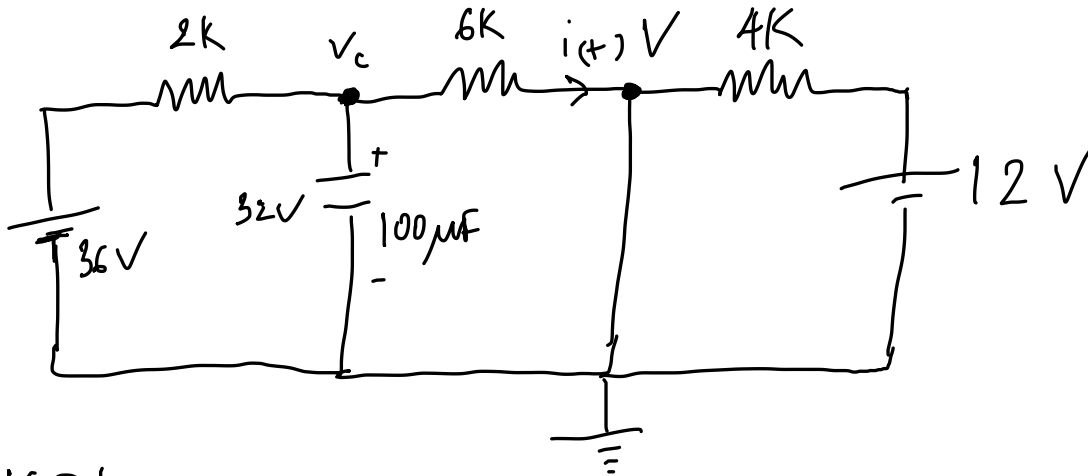


KCL:

$$\Rightarrow V = 0 \text{ V} \Rightarrow i = i(0^+) = \frac{V_c - V}{6 \text{ k}\Omega} = \frac{32 \text{ V} - 0}{6 \text{ k}\Omega}$$

$$\Rightarrow i = i(0^+) = \boxed{\frac{16}{3} \text{ (mA)} \approx 5.33 \text{ (mA)}}$$

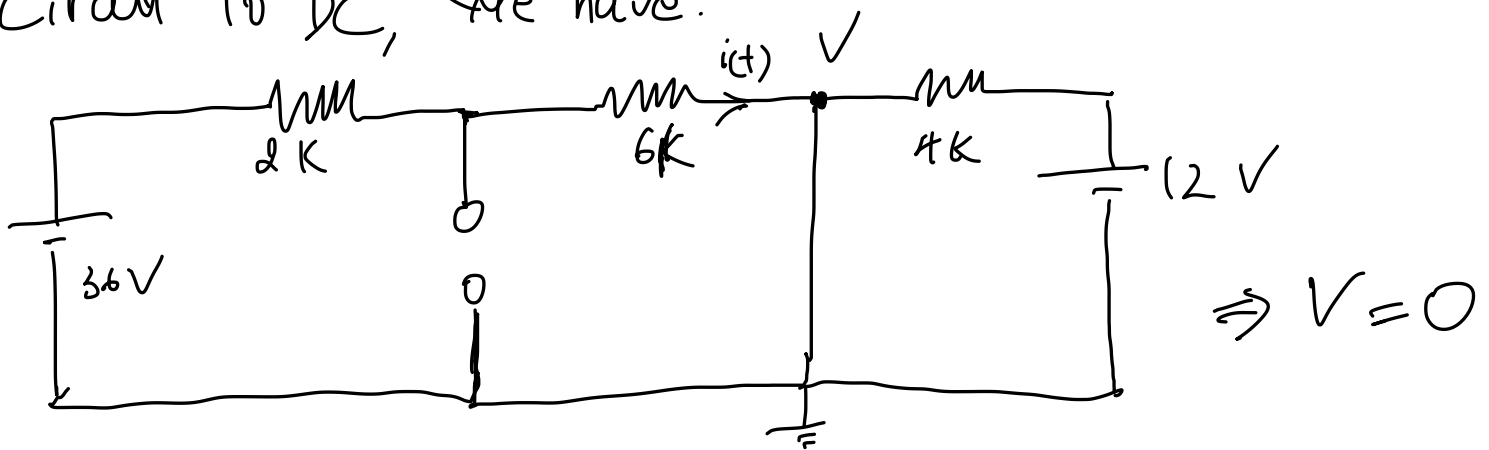c) After closing the switch, the capacitor will be discharged, so when $t \rightarrow \infty$, the capacitor is opened circuit to DC, we have:




$$\Rightarrow V = 0$$


We have $i = \frac{36 - V}{2k\Omega + 6k\Omega} = \frac{36 - 0}{8k\Omega} = \frac{36V}{8k\Omega}$

$\rightarrow i = i(\infty) = 4.5(mA)$

d) When $t > 0$, we have the circuit:

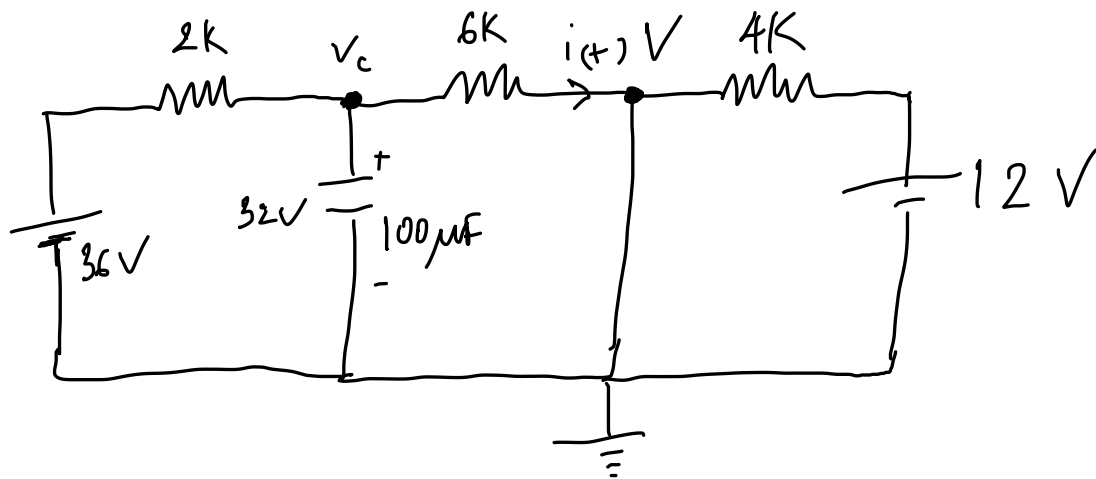

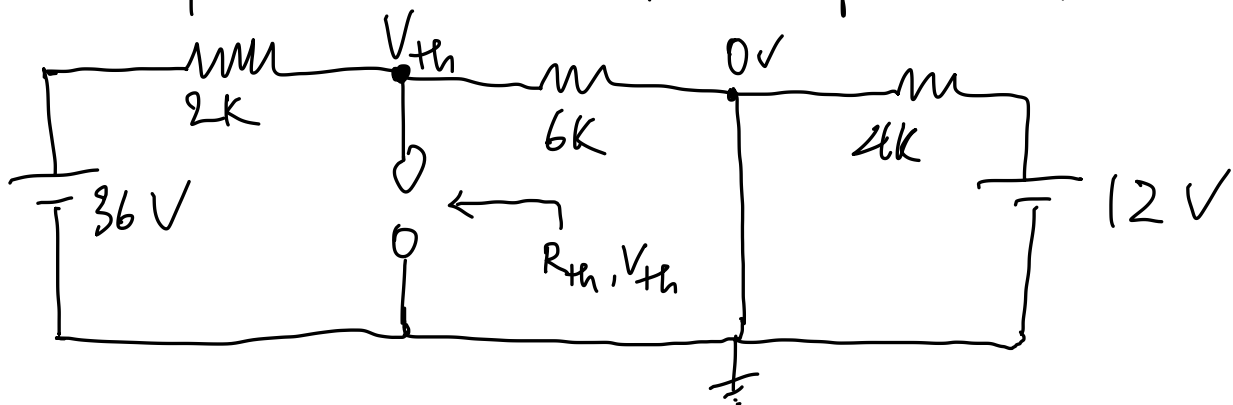⊕ Firstly, we can apply the Thévenin equivalent, and the ports are at the capacitors.



* We find the V_{th} .

$$\frac{V_{th} - 36}{2k} + \frac{V_{th} - 0}{6k} = 0$$

$$\Rightarrow 3(V_{th} - 36) + V_{th} = 0 \Leftrightarrow 3V_{th} + V_{th} = 3 \times 36$$

$$\Rightarrow 4V_{th} = 108(V) \Rightarrow V_{th} = 27(V)$$


* Find R_{th} .

Because we only have independent source, so we can short the voltage sources, so:



$$\Rightarrow R_{th} = 2k \parallel 6k = \frac{2 \times 6}{2 + 6} = 1.5(k\Omega)$$

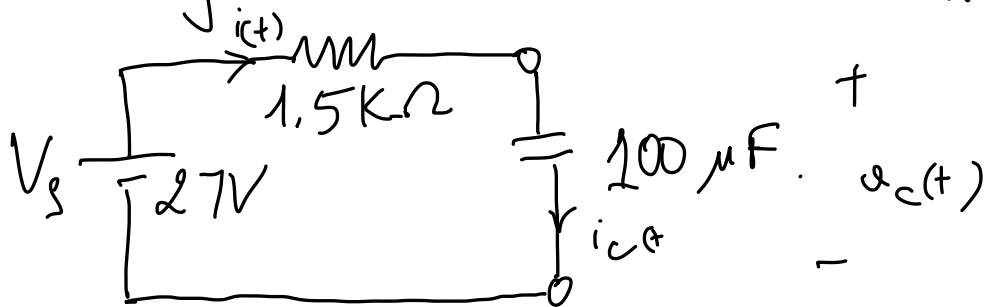Finally we can have the Thévenin equivalent circuit:



From there, we apply the equation for RC circuit in third slide of Lecture 4 in Week 4, we have

$$v_c(t) = V_s - [V_s - v_c(0^+)] e^{-t/RC}$$

$$\text{Also, at } t \rightarrow 0^+, v_c = 32V, RC = 1.5 \times 1000 \times 100 \times 10^{-6} = 0.15(s)$$

$$\Rightarrow v_c(t) = 27 - (27 - 32) e^{-t/0.15}$$

$$\Rightarrow v_c(t) = 27 + 5 e^{-\frac{20}{3}t} \quad (V)$$

(*) We can prove at below:

$$-27 + 1.5K i(t) + v_c(t) = 0, \quad v_c(0^+) = 32(V)$$

$$\Leftrightarrow 1.5K \cdot C \cdot \frac{dv_c}{dt} + v_c(t) = 27(V)$$

$$\Leftrightarrow 1.5KC \cdot \frac{dv_c}{dt} = -v_c + 27$$

$$\Leftrightarrow \int \frac{dv}{27 - v_c} = \int \frac{dt}{1.5KC} \quad \Leftrightarrow \int \frac{dv}{v_c - 27} = - \int \frac{dt}{1.5KC}$$

$$\Leftrightarrow \ln(v_c - 27) \Big|_{v_0=32V, t \rightarrow 0^+}^{v_t} = \frac{-t}{1.5KC} \quad \Leftrightarrow \ln \frac{v_t - 27}{32 - 27} = \frac{-t}{1.5KC} \Big|_{0^+}^t$$

$$\Leftrightarrow \ln \frac{v_t - 27}{5} = \frac{-t}{1.5K \cdot C} = \frac{-t}{1.5 \times 1000 \times 100 \times 10^{-6}} = \frac{-t}{0.15}$$


$$\Rightarrow v_t - 27 = 5 e^{-\frac{20}{3}t}$$

$$\Rightarrow v_c(t) = 27 + 5 e^{-\frac{20}{3}t} \quad (V)$$

$$\Rightarrow \frac{dv_c(t)}{dt} = 5 \cdot \left(-\frac{20}{3}\right) e^{-\frac{20}{3}t} = -\frac{100}{3} e^{-\frac{20}{3}t} \quad (V)$$

$$\Rightarrow i_c(t) = C \frac{dV_c(t)}{dt} = 100 \times 10^{-6} \times -\frac{100}{3} e^{-\frac{20}{3}t}$$
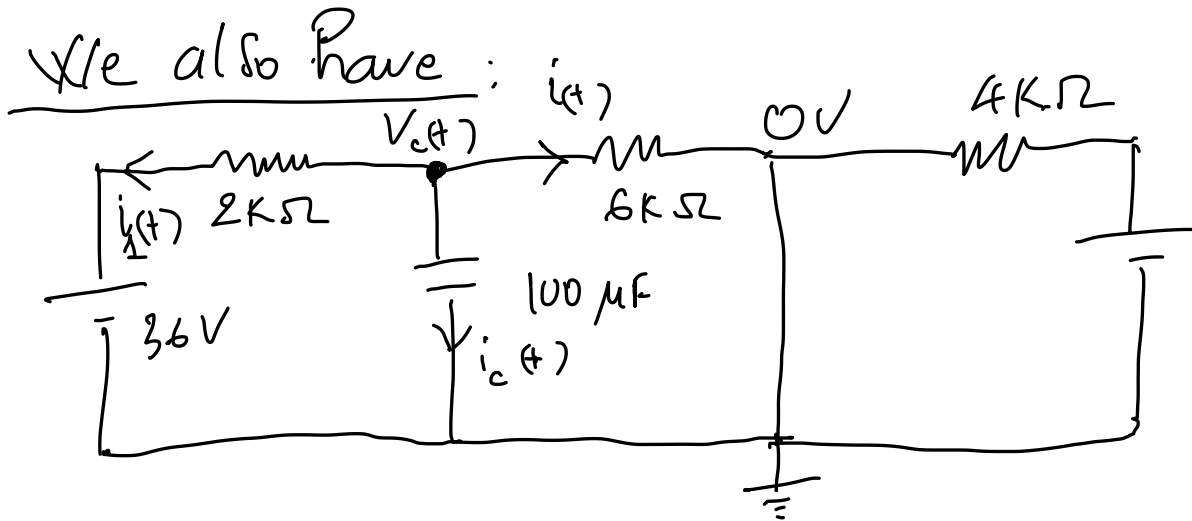
$$= -\frac{1}{300} e^{-\frac{20}{3}t} \text{ (A)} = -\frac{10}{3} e^{-\frac{20}{3}t} \text{ (mA)}$$




$$\Rightarrow i(t) = \frac{V_c(t) - 0V}{6k\Omega} \text{ (mA)}$$

$$= \frac{27 + 5e^{-\frac{20}{3}t} \text{ (V)}}{6k\Omega}$$

$$\Rightarrow i(t) = \frac{27 + 5e^{-\frac{20}{3}t}}{6} \text{ (mA)} (t > 0)$$

(+) Secondly, instead of using Thevenin, we can solve this problem by using a differential equation, then compare the result.

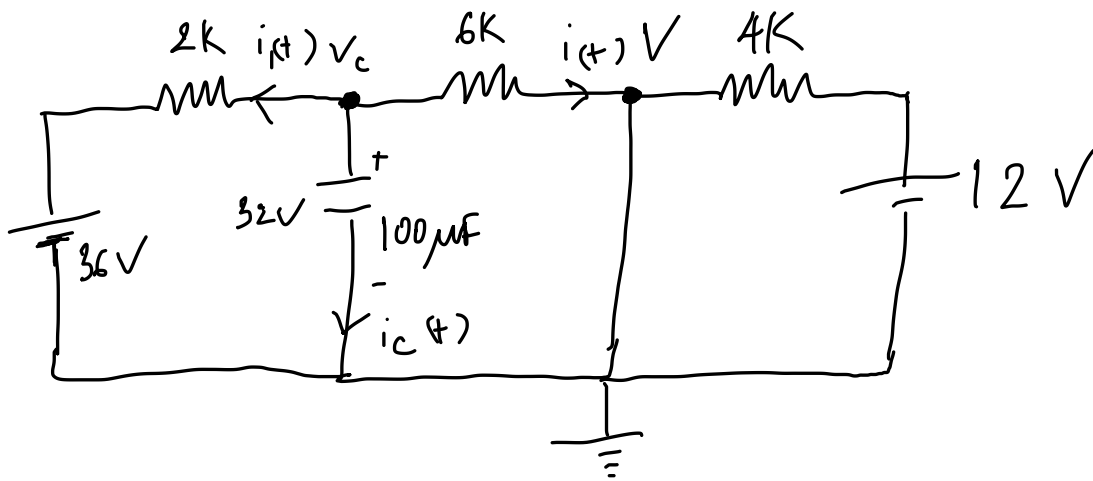We have: At $t = 0^+$, $V_c(t) = V_0 = 32(V)$



$$\frac{V_c - 36}{2K} + i_c + \frac{V_c - 0}{6K} = 0$$

$$\Leftrightarrow 3(V_c - 36) + 6K \cdot i_c + V_c = 0$$

$$\Leftrightarrow 3V_c + V_c + 6i_c = 108(V)$$

$$\Leftrightarrow 4V_c + 6i_c = 108 \Leftrightarrow 4V_c + 6C \frac{dV_c}{dt} = 108$$

$$\Leftrightarrow 6K \cdot C \frac{dV_c}{dt} = 108 - 4V_c$$

$$\Leftrightarrow 1.5K \cdot C \frac{dV_c}{dt} = 27 - V_c$$

$$\Leftrightarrow \frac{dV_c}{27 - V_c} = \frac{dt}{1.5K.C} \Leftrightarrow \int \frac{dV_c}{V_c - 27} = - \int \frac{dt}{1.5K.C}$$

$$\Leftrightarrow \ln(V_c - 27) \Big|_{V_0}^{V_c(t)} = \frac{-t}{1.5K.C} \Big|_0^t$$

$$\Leftrightarrow \ln \frac{V_c(t) - 27}{32 - 27} = \frac{-t}{1.5K.C}$$

$$\Leftrightarrow V_c(t) = 27 + 5 e^{-\frac{t}{1.5K.C}}$$

$$\text{Also, } 1.5K.C = 1.5 \times 1000 \times 100 \times 10^{-6} = 0.15(s)$$

$$\Leftrightarrow V_c(t) = 27 + 5 e^{-\frac{20}{3}t} \quad (V)$$

$$\Rightarrow i(t) = \frac{V_c(t) - 0}{6K} = \frac{27 + 5 e^{-\frac{20}{3}t}}{6K} \quad (mA)$$

$$\Rightarrow i(t) = \frac{27 + 5 e^{-\frac{20}{3}t}}{6} \quad (mA)$$

As we can see, with 2 ways of solution we have

$$t > 0, \quad i(t) = \frac{27 + 5 e^{-\frac{20}{3}t}}{6} \quad (mA) = \frac{27 + 5 e^{-\frac{20}{3}t}}{6000} \quad (A)$$