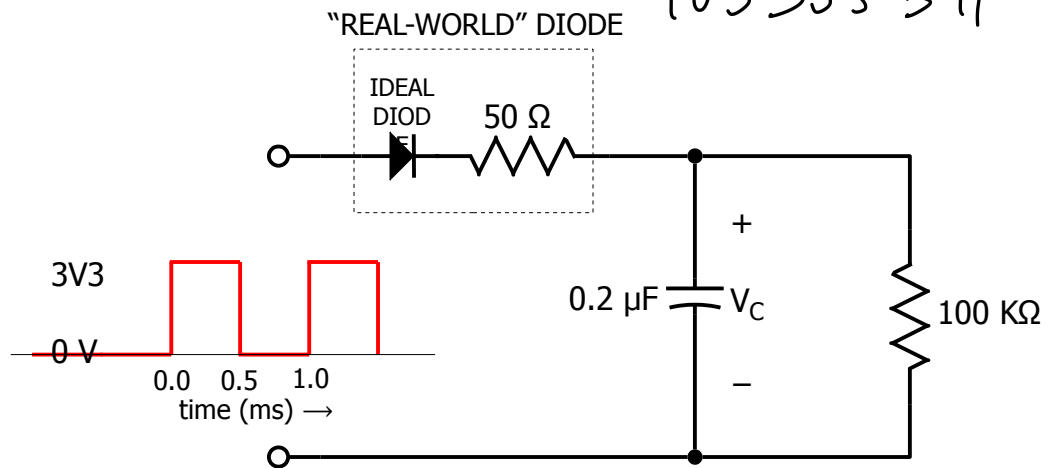


EE3 Fall 2020
Homework Problem 4

Nhat Ho


105355311



The input voltage has been at 0 V for a long time. All transients have died out. At time $t = 0.0$, a 3V3 pulse train begins. NOTE: the device inside the dashed-line box is an approximation of a real-world diode: when the left end is positive with respect to the right end, it is **forward-biased** and its resistance is 50 Ω . When the left end is negative, it is **reverse-biased** and its resistance is ∞ .

- When the input voltage is 3V3, the diode is forward-biased; $3V3 > v_c$. What is the charging time constant? Neglect the effect of the 100 k Ω resistor.
- When the input voltage is 0 V, the diode is reverse-biased, $v_c > 0$ V, and the capacitor can discharge only through the 100 k Ω resistor. What is the discharging time constant?
- What is v_c at time 0.0+?
- What is v_c at time 0.5+? You will need to evaluate the equation describing the behavior as shown on Slide 3 of Lecture 4 on CCLE Week 3.
- What is v_c at time 1.0+? Remember that v_c cannot change in the transition from 0- to 0+.
- Based on what you see in (d.) and (e.), predict the value of v_c at time 1.5+.

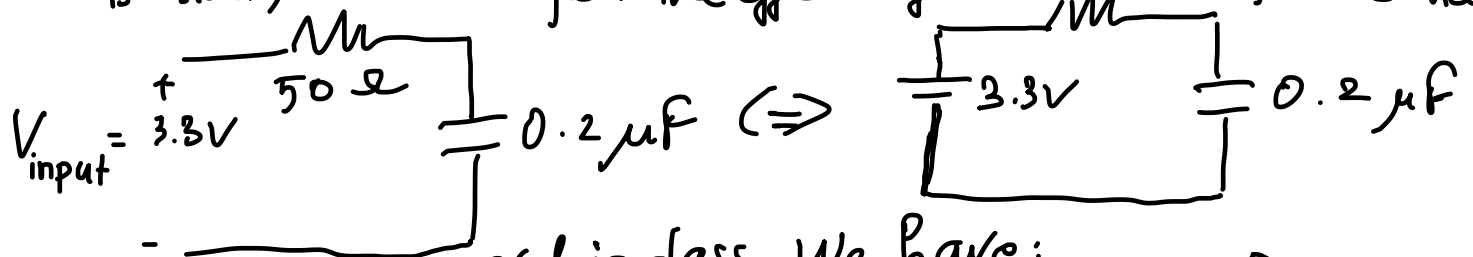
a) Because when $V_{input} = 3.3$ V, the forward-biased happens and at this time, the capacitor will be charged by the V_{input} . Besides, we can neglect the effect of the 100 k Ω , so we have:




As we proved in class, we have:

$$\Rightarrow \tau = RC = 50 \Omega \times 0.2 \times 10^{-6} = 10^{-5} \text{ (s)}$$

$$\Rightarrow \text{charging time constant: } \boxed{\tau = 10^{-5} \text{ (s)}}$$

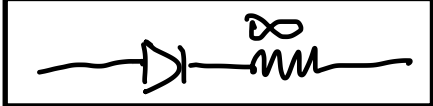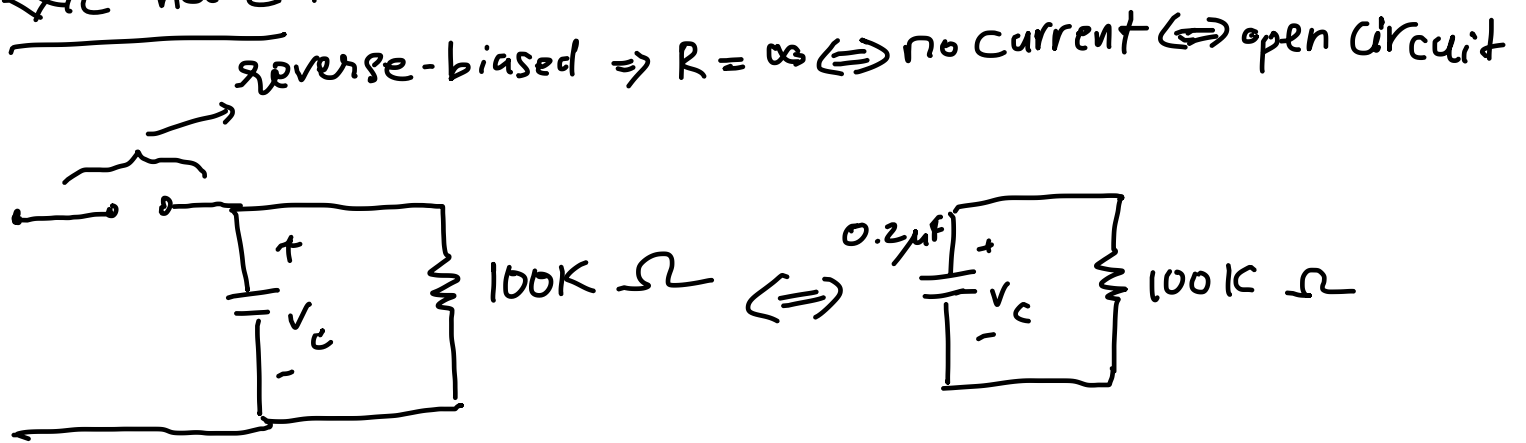
b) When the input $V = 0V$, the diode is reverse biased, at that time, the resistance of diode is ∞ . So, the capacitor can discharge only through the $100K\Omega$ resistor, \Rightarrow we have:



$$\Rightarrow \tau = RC = 100 \times 1000 \times 0.2 \times 10^{-6}$$

$$\Rightarrow \boxed{\tau = 0.02 (s)}$$

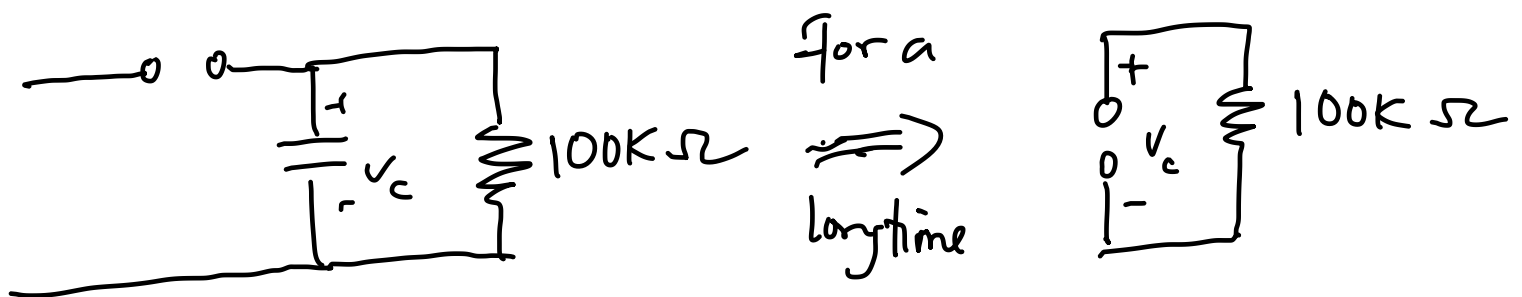c) Because the input voltage has been at $0V$ for a long time, so at $t = 0^-$ we have:




$\Rightarrow V_c(0^-) = 0V$. Since the voltage of capacitor can not change instantaneously

$$\Rightarrow \boxed{v_c(0^+) = 0 \text{ V}}$$

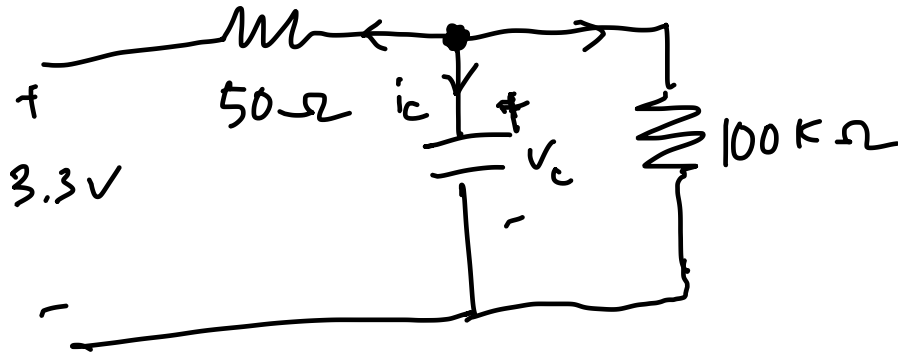d) Find v_c at $t = 0.5^+$

At $t = 0^+ \rightarrow 0.5^-$, $v_{\text{input}} = 3.3 \text{ V} > v_c$, we have:



We have known already $v_c(0^+) = 0 \text{ V}$

We have:

$$\frac{v_c - 3.3 \text{ V}}{50 \Omega} + i_c + \frac{v_c}{100000 \Omega} = 0 \text{ (KCL)}$$

$$\Rightarrow \frac{2000(v_c - 3.3 \text{ V}) + v_c}{100000 \Omega} + C \frac{dv_c}{dt} = 0$$

$$\Rightarrow \frac{2001 v_c - 6600 \text{ V}}{100000 \Omega} + \frac{0.2 \times 10^{-6} \times 100000 \frac{dv_c}{dt}}{100000 \Omega} = 0$$

$$\Rightarrow 2001 v_c - 6600 = -0.02 \frac{dv_c}{dt}$$

$$\Rightarrow \frac{dv_c}{2001 v_c - 6600} = -50 dt$$

$$\Rightarrow \frac{dv_c}{v_c - \frac{6600}{2001}} = -50 \times 2001 dt$$


$$\Rightarrow \int \frac{dV_c}{V_c - \frac{6600}{2001}} = \int (-100050) dt$$

$$\Rightarrow \ln \frac{V_c - \frac{6600}{2001}}{0 - \frac{6600}{2001}} = -100050 t$$

$$\Rightarrow V_c - \frac{6600}{2001} = - \frac{6600}{2001} e^{-100050 t}$$

$$\Rightarrow V_c = \frac{6600}{2001} - \frac{6600}{2001} e^{-100050 t}$$
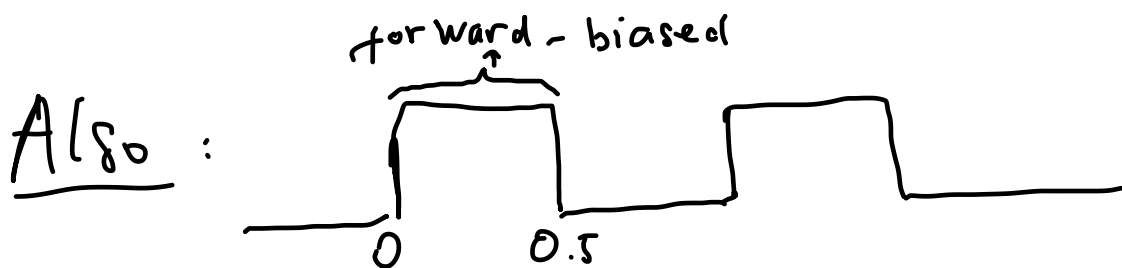
$$\Rightarrow V_c(t) = \frac{6600}{2001} (1 - e^{-100050 t}) \quad (\checkmark)$$



\Rightarrow From $t = 0^+ \rightarrow t = 0.5^-$

We will have the voltage of capacitor will follow

$$V_c(t) = \frac{6600}{2001} (1 - e^{-100050t}) (V)$$


$$\Rightarrow V_c(t) = \frac{2200}{667} (1 - e^{-100050t}) (V)$$

$$\Rightarrow \text{at } t = 0.5^-,$$

$$V_c = \frac{6600}{2001} (1 - e^{-100050 \times 0.5})$$

$$\Rightarrow V_c(0.5^-) \approx \frac{6600}{2001} \approx 3.298(V)$$

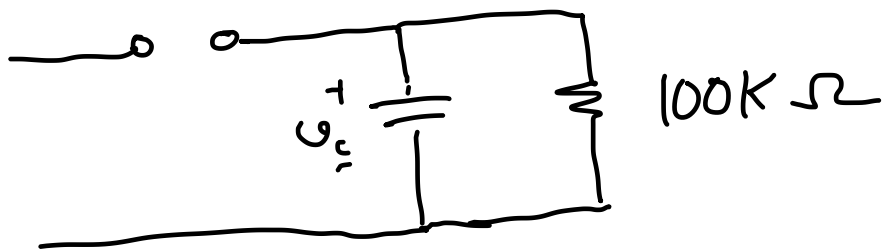At $t = 0.5^+$, the voltage input begins equal 0 \Rightarrow reverse-biased happens again. We have:




Because the voltage of capacitor cannot change instantaneously \rightarrow $V_c(0.5^-) = V_c(0.5^+) = 3.298V$

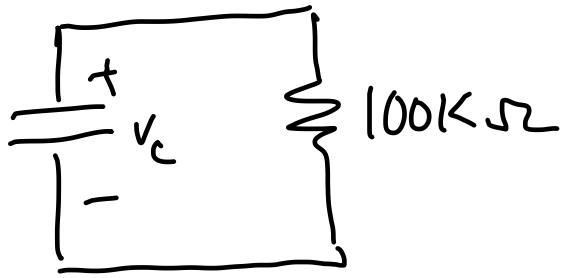e) As we can see, start from $t = 0.5^+$, the reverse-biased happens again that makes

the capacitor discharge, and we have:

$t = 0.5^+ \rightarrow 1^- \Leftrightarrow$ capacitor discharge:



$$V_c(0.5^+) = 3.298(V)$$

In this basic RC circuit

We have: $\tau = RC = 100 \times 10^3 \times 0.2 \times 10^{-6}$

$$\Rightarrow \tau = 0.02$$

$$V_c + iR = 0 \Leftrightarrow V_c + C \frac{dV_c}{dt} R = 0$$

$$\Rightarrow V_c = -RC \frac{dV_c}{dt} \Leftrightarrow \frac{dV_c}{V_c} = -\frac{1}{RC} dt$$

$$\Leftrightarrow \int_{0.5^+}^t \frac{dV_c}{V_c} = \int_{0.5^+}^t -\frac{1}{RC} dt \Leftrightarrow \ln V_c \Big|_{0.5^+}^t = \frac{-t}{RC} \Big|_{0.5^+}^t$$

$$\Leftrightarrow \ln \frac{V_c(t)}{V_c(0.5^+)} = -\frac{1}{RC} (t - 0.5^+)$$

$$\Leftrightarrow \ln \frac{V_c(t)}{3.298V} = -50(t - 0.5^+)$$

$$\Rightarrow V_c(t) = 3.298 \times e^{-50(t - 0.5^+)} (V)$$

$$\text{at } t = 1^- \Rightarrow V_c(1^-) = 3.298 \times e^{-50 \times 0.5}$$

$$\Rightarrow V_c(1^-) = 4.58 \times 10^{-11} \text{ (V)} \approx 0 \text{ (V)}$$

$$\Rightarrow \text{at } t = 1^-, V_c = 0 \text{ (V)}.$$

$$\Rightarrow \text{at } t = 1^+, \boxed{V_c(1^+) = V_c(1^-) = 0 \text{ V}}$$

because the voltage of capacitor can not change instantaneously.



From part d & e, we realize the capacitor will be charged and discharged continuously with the same period 0.5s.

Particularly, in 0.5s from $0^+ \rightarrow 0.5^-$, the capacitor will be charged to have $V_c \approx 3.298 \text{ (V)}$, and then it will be discharge from $0.5^+ \rightarrow 1^-$ to have $V_c \approx 0 \text{ (V)}$.

Similarly, from $t = 1^+ \rightarrow 1.5^-$, the capacitor will be continued charged to have $V_c(1.5^-) = 3.298(V)$. Then, we can predict the voltage of capacitor at $t = 1.5^+$ equal V_c at $t = 1.5^-$

$$\Rightarrow V_c(1.5^+) = V_c(1.5^-) = \boxed{3.298(V)}$$