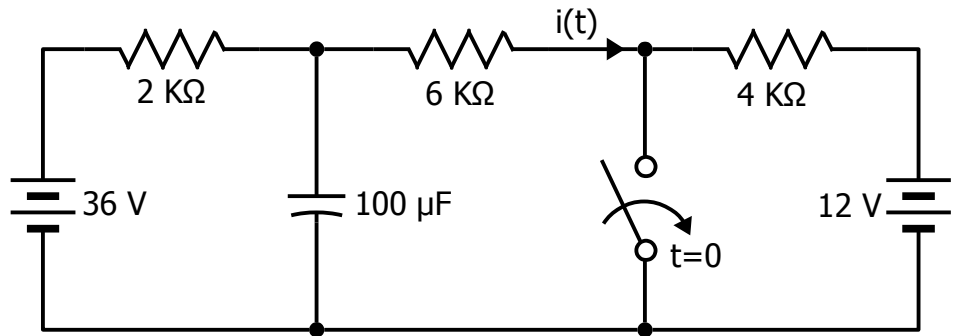


EE3 Fall 2020

Homework Problem 6

This problem is all about $i(t)$.

- a. What is $i(0^-)$?
- b. What is $i(0^+)$?
- c. What is $i(\infty)$?
- d. What is $i(t)$, $t > 0$?



The circuit has been in this condition for a long time.

This problem can be solved without using a differential equation, though you may do so this way if you wish. Solving it without using a differential equation is done by pulling together a few ideas and bringing them to bear on the problem. That means using the answers to the first 3 parts of this problem, plus the judicious use of a Thévenin equivalent, plus the third slide of Lecture 4 in Week 4 of CCLE.