Family (Last) Name

Given (First) Name

The switch has been in position 1 for a <u>long time</u>. At t=0, the switch move instantaneously to position 2. Find:

a. $v_c(0+)$

b. v_c(Long Time)

