


ECE3 FALL QUARTER 2020 LECTURE 5

MAXIMUM POWER TRANSFER

RESLK SENSOR CALIBRATION


SINUSOIDAL STEADY-STATE (SSS) AC CIRCUITS

MAXIMUM POWER TRANSFER

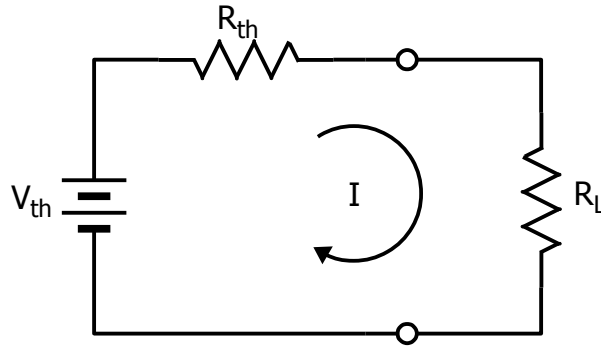

What value of R_L maximizes power to R_L (P_{RL})?
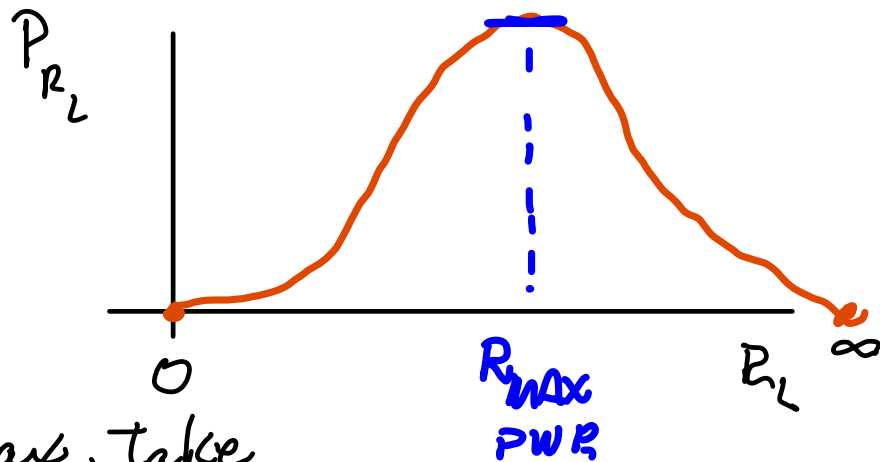
$$P_{R_L} = I^2 R_L = \left(\frac{V_{th}}{R_{th} + R_L} \right)^2 R_L$$



To find max, take derivative & set = 0.

$$\left. \frac{dP_{R_L}}{dR_L} \right|_0 = \left. \frac{d}{dR_L} \left[\left(\frac{V_{th}}{R_{th} + R_L} \right)^2 R_L \right] \right|_0$$

$R_L = R_{th}$ for max power to R_L .

IMPEDANCE
MATCHING

RSLK SENSOR CALIBRATION

TAKING PATH SENSOR CALIBRATION MEASUREMENTS

<https://youtu.be/swOMZOSCpzM>

SENSOR FUSION EXPLANATION

<https://youtu.be/KrjccJ-EVjE>

SINUSOIDAL STEADY-STATE (SSS) AC CIRCUITS

Why sinusoidal?
Why Steady-State?
Complex Representation
The Complex Plane
AC Voltages and Currents
Complex to Real World
Impedance
Impedance Forms
Impedance vs V/I Phasors
SSS Calculations
Inductive Reactance Derivation
Circuit Analysis


LECTURE 6

Frequency Response
Resonance
Filters
Cutoff Frequency
Filter Types

WHY SINUSOIDAL?

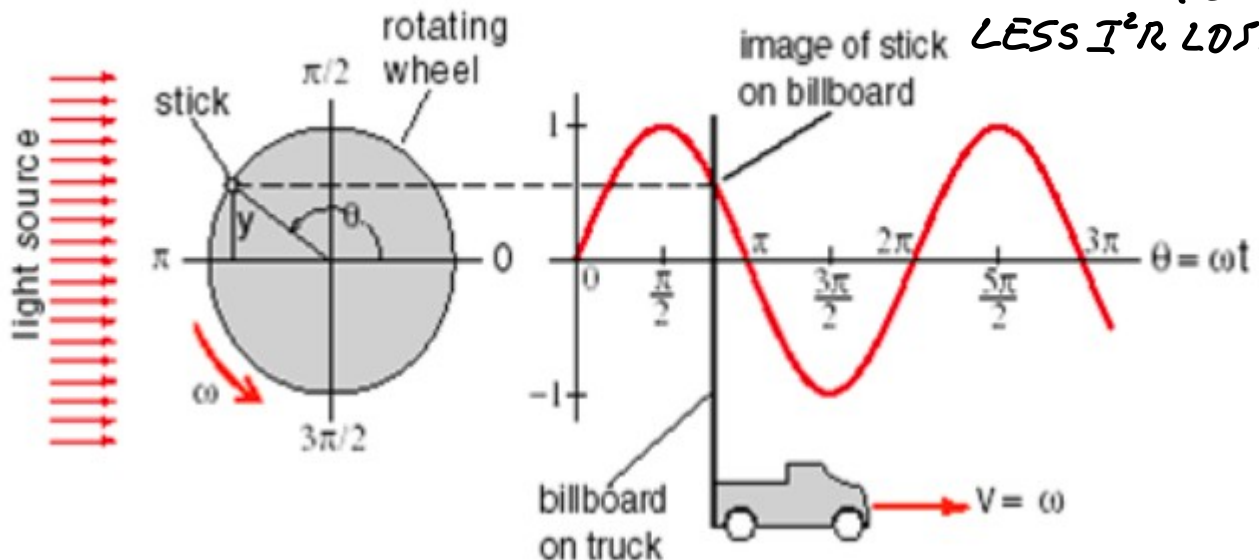1. Circular motion makes sinusoids


- GENERATORS
- HIGH VOLTAGES FOR LONG LINES: LESS I^2R LOSS.



2. Fourier Series

Any repetitive waveform can be represented by a (possibly infinite) series of sinusoids of varying amplitude.

➤ Square wave

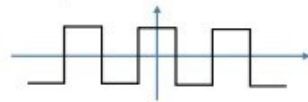

$$\frac{4A}{\pi} \left(\cos \omega_1 t - \frac{1}{3} \cos 3\omega_1 t + \frac{1}{5} \cos 5\omega_1 t - \frac{1}{7} \cos 7\omega_1 t + \dots \right)$$

➤ Triangular wave



$$\frac{8A}{\pi^2} \left(\cos \omega_1 t + \frac{1}{9} \cos 3\omega_1 t + \frac{1}{25} \cos 5\omega_1 t + \dots \right)$$

➤ Sawtooth wave



$$\frac{2A}{\pi} \left(\sin \omega_1 t - \frac{1}{2} \sin 2\omega_1 t + \frac{1}{3} \sin 3\omega_1 t - \frac{1}{4} \sin 4\omega_1 t + \dots \right)$$

WHY STEADY-STATE?

Steady-state is main operating mode for many use cases, where efficiency is important.

1. HVAC -- heating, ventilation, & air conditioning
2. Some electric cars: Tesla, Chevy Bolt
3. Wireless communications

ALSO:

4. Calculations are easy (no differential equations!)


COMPLEX REPRESENTATION

$$\sqrt{-1} = j$$

Complex #s:

- Eulerian: $e^{j\theta}$
- Cartesian } $a + jb$
Rectangular }
- Polar: $c \angle \theta$

THE COMPLEX PLANE

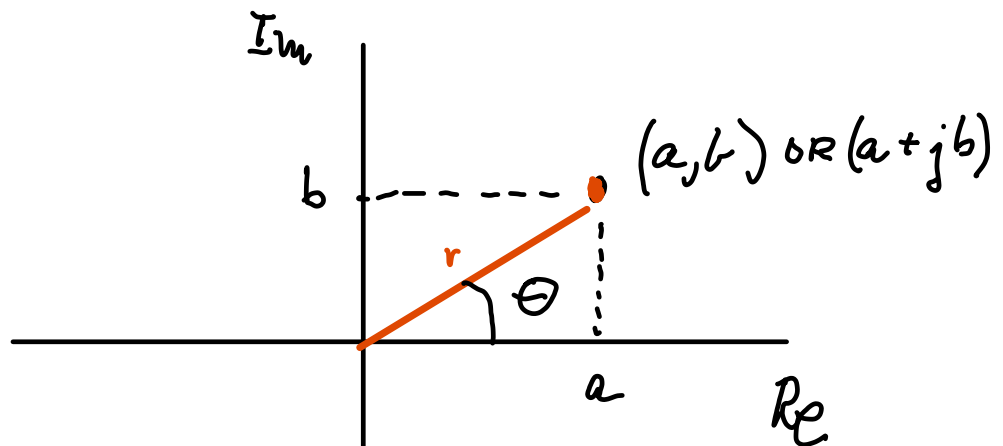

$$r^2 = a^2 + b^2$$


$$\theta = \tan^{-1} \frac{b}{a}$$

COMPLEX TO REAL WORLD

$$v(t) = C e^{j\theta} = a + jb = C \angle \theta$$

$$j\theta = j\omega t \quad \omega: \text{rad/s} \quad t: \text{s}$$
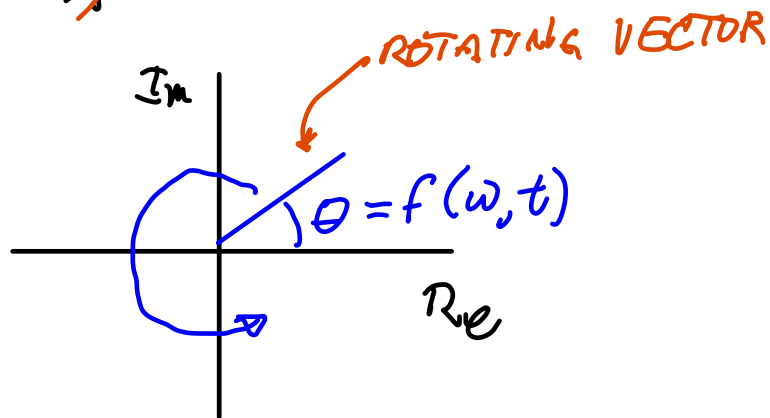
$$\cancel{\text{rad}}/\cancel{\text{s}} \times \cancel{\text{s}} = \text{rad}$$



So, for a given frequency ω ,
 $v(t)$ can be written as

$$v(t) = C \cos(\omega t + \theta)$$

ALL REAL #'S!

IMPEDANCE

A superset of resistance.


IMPEDANCE (Z)

- Resistance (R)
- Reactance (X, X_L, X_C)
 inductive capacitive
- Reactive Impedance (Z_L, Z_C)

It is convenient to represent impedance as a complex-number quantity.

$$Z = R + jX$$

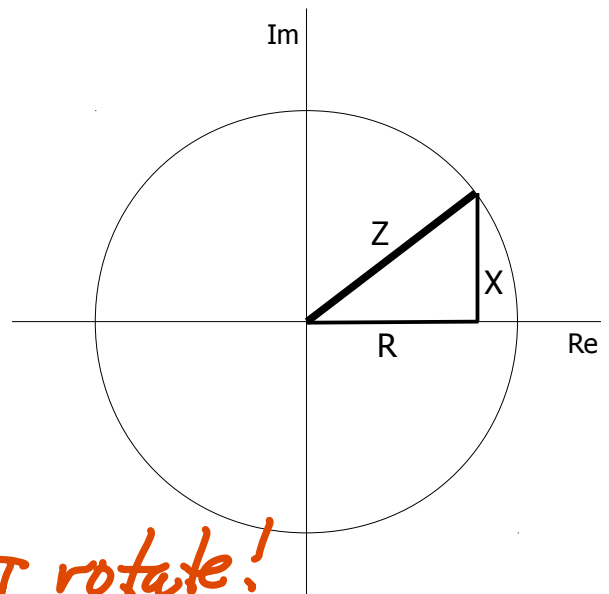*Z is a
constant.
Vector does NOT rotate!*



REACTANCE, REACTIVE IMPEDANCE, AND IMPEDANCE

Reactance: **REAL #**

$$\text{Ex: } X_C = \frac{1}{\omega C}$$

$$X_L = \omega L$$

Reactive Impedance **IMAGINARY #**

$$\text{Ex: } Z_C = \frac{1}{j\omega C} = -j\left(\frac{1}{\omega C}\right)$$

$$Z_L = j\omega L$$

Impedance **COMPLEX #**

$$\text{Ex: } Z = R + jX$$

$$Z = R - j\left(\frac{1}{\omega C}\right)$$



$$Z = R + j\omega L$$

IMPEDANCE vs PHASORS

Both are complex.

Impedances represent **CONSTANT** quantities,

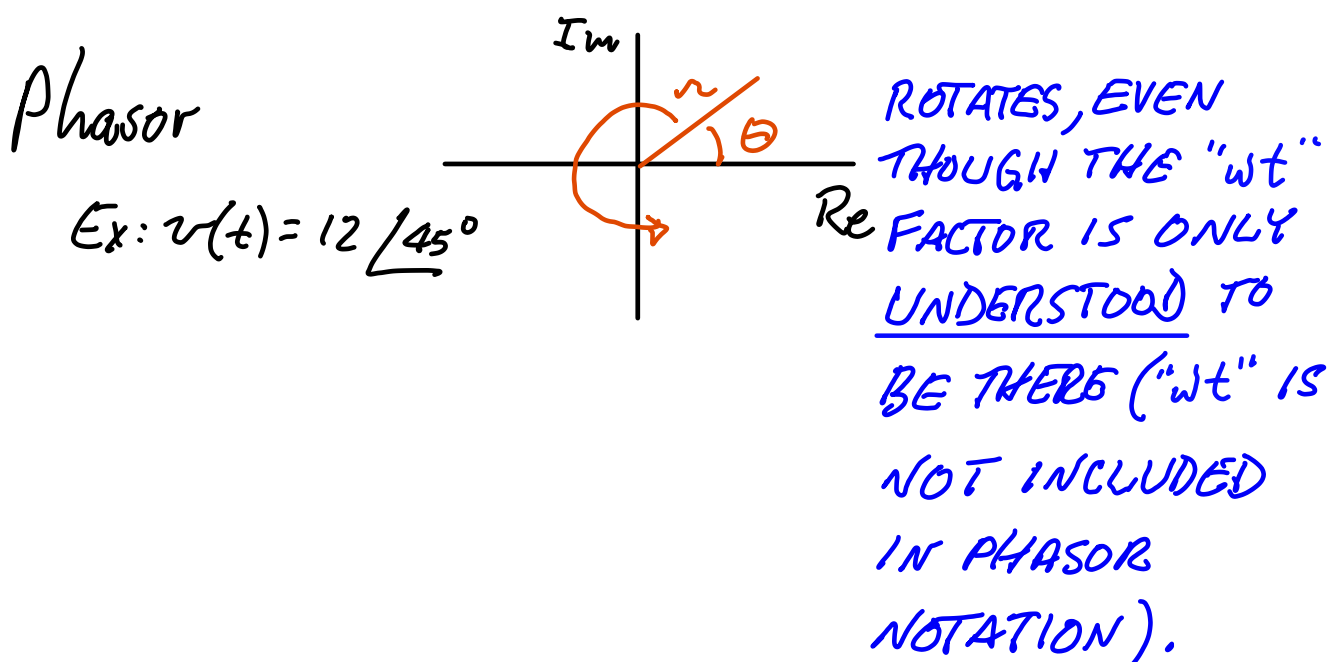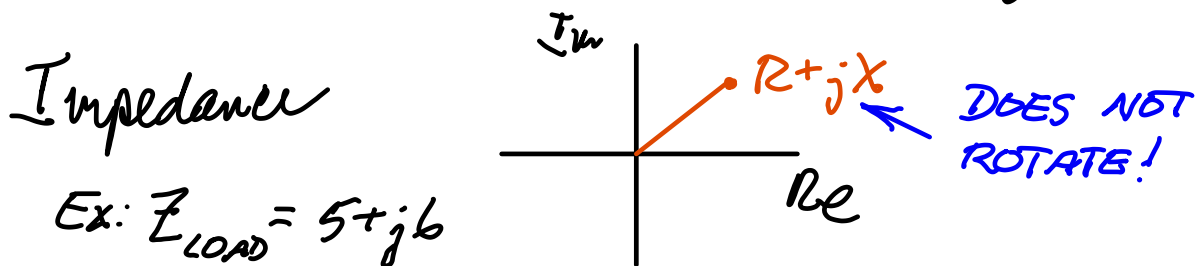Phasors represent **TIME-VARYING** quantities.




SSS CALCULATIONS

All ckt calculations in SSS are the same as for DC except the calculations use complex #'s. Only complex arithmetic.

REACTIVE IMPEDANCE DERIVATION

Let $i(0) = i_0$

Let $v(t) = e^{j\omega t}$

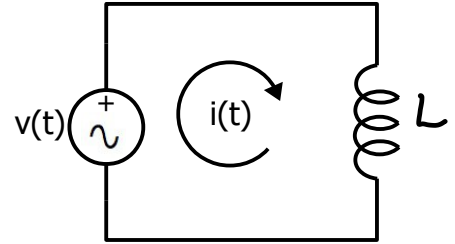

We want $X_L = \frac{v(t)}{i(t)}$

$$-e^{j\omega t} + L \frac{di}{dt} = 0$$

Guess: $i(t) = A e^{st}$ $\frac{di}{dt} = A s e^{st}$

$$i(0) = i_0 = A e^0 = A$$

$$e^{j\omega t} = L i_0 s e^{st} \Rightarrow s = j\omega \text{ [by similarity of exponents]}$$


$$e^{j\omega t} = L i_0 j\omega e^{j\omega t} \Rightarrow 1 = L i_0 j\omega \Rightarrow i_0 = \frac{1}{j\omega L}$$

So $A = \frac{1}{j\omega L}!$

Apply to guess: $i(t) = A e^{j\omega t} = \frac{1}{j\omega L} e^{j\omega t}$

$$X_L = \frac{v(t)}{i(t)} = \frac{e^{j\omega t}}{\frac{e^{j\omega t}}{j\omega L}} = j\omega L$$

VOILA!

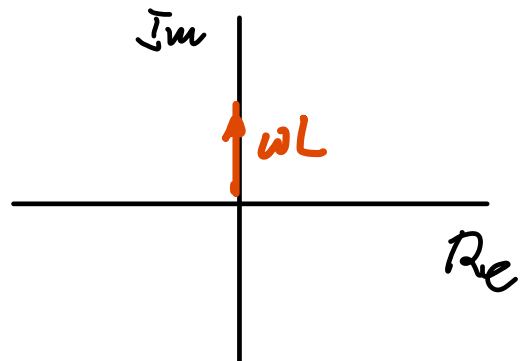


SIMPLE CIRCUIT ANALYSIS

$$Z_C = -j\left(\frac{1}{\omega C}\right) = -j\left(\frac{1}{(10^3)(20 \times 10^{-6})}\right)$$

$$Z_C = -j50$$

$$Z_L = j\omega L = j100$$

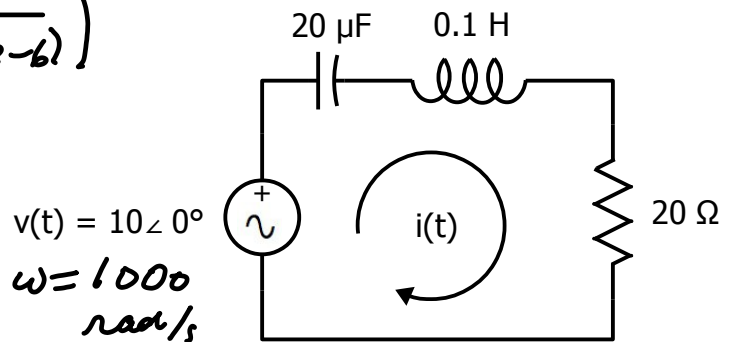

$$\text{KVL: } -10 \angle 0^\circ + \dot{i} Z_C + \dot{i} Z_L + \dot{i} R = 0$$


$$Z_{\text{TOT}} = -j50 + j100 + 20 = 20 + j50$$

$$\dot{i} Z_{\text{TOT}} = \dot{i} (20 + j50) = 10 \angle 0^\circ$$


$$\dot{i} = \frac{10 \angle 0^\circ}{20 + j50} \approx 0.18 \angle -68^\circ$$

**LEARN TO DO THIS
ON YOUR CALCULATOR
IN YOUR SLEEP!**

IMPEDANCES

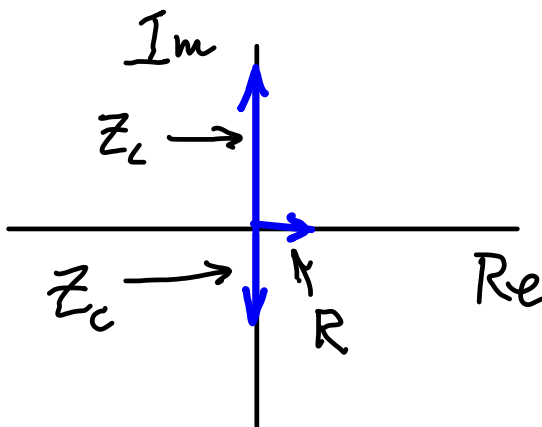


PHASORS

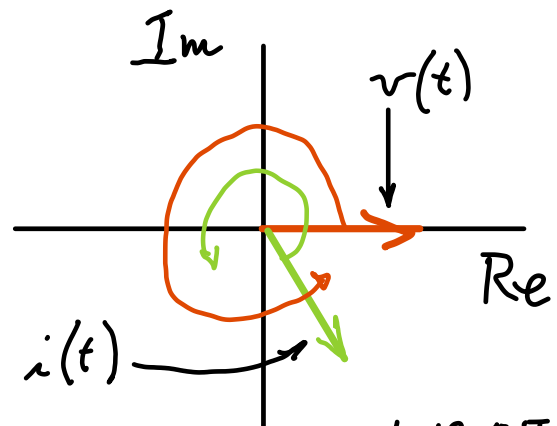

BOTH VOLTAGE & CURRENT
PHASORS ROTATE AT
1000 RAD/S.
CURRENT LAGS BEHIND
VOLTAGE.

AC NODE-VOLTAGE CIRCUIT ANALYSIS

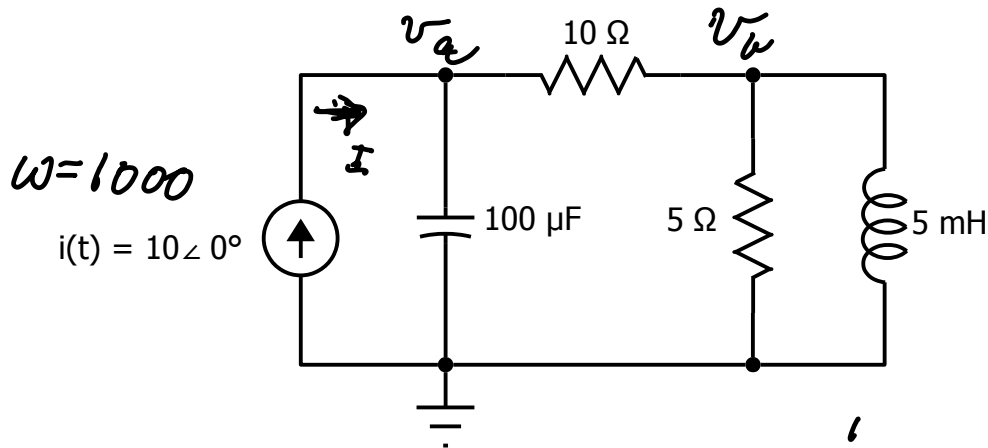

$$Z_L = j(10^3)(5 \times 10^{-3}) = +j5 \quad Z_C = \frac{1}{j(10^3)(100 \times 10^{-6})} = -j10$$

$$\begin{aligned} -I + \frac{v_a}{-j10} + \frac{v_a - v_b}{10} &= 0 \\ \frac{v_b - v_a}{10} + \frac{v_b}{5} + \frac{v_b}{j5} &= 0 \end{aligned}$$

$$\begin{aligned} \left(\frac{-j10}{-j10} \right) (-10) + \frac{v_a}{(-j10)} + \left(\frac{-1}{-j} \right) \frac{v_a - v_b}{10} &= 0 \\ \left(\frac{1}{j} \right) \frac{v_b - v_a}{10} + \left(\frac{2j}{5} \right) \frac{v_b}{5} + \left(\frac{2}{j5} \right) \frac{v_b}{5} &= 0 \end{aligned}$$

$$\begin{aligned} -j100 - v_a + j(v_a - v_b) &= 0 \\ j(v_b - v_a) + j2v_b + 2v_b &= 0 \end{aligned}$$

$$\begin{aligned} (-1+j)v_a - jv_b &= j100 \\ -jv_a + (2+j3)v_b &= 0 \end{aligned}$$

$$\begin{aligned} v_a &= 58.8 - j64.7 = 87.5 \angle -47.7^\circ \\ v_b &= 23.5 - j5.9 = 24.3 \angle 166^\circ \end{aligned}$$