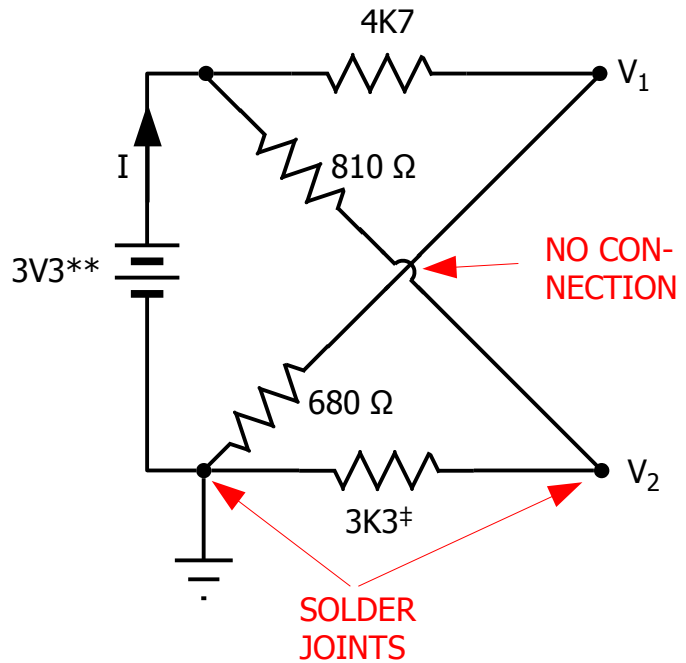


ECE3 Fall 2020  
Quiz 2

Name \_\_\_\_\_  
Family (Last) Name                      Given (First) Name

You saw almost the same circuit in Practice Problems 1. This time write (DO NOT SOLVE) the Node Voltage Analysis equations for Nodes  $V_1$  and  $V_2$ .



† 3K3 is shorthand for  $3.3\text{K}\Omega$ . You will see this often on schematics.

\*\* 3V3 is shorthand for 3.3 V