

ECE3 Fall 2020
Quiz 4

Name _____ | _____
Family (Last) Name Given (First) Name

Find the Thévenin Equivalent circuit to the left of the capacitor. That is, consider the capacitor to be the load on the entire circuit to its left.

