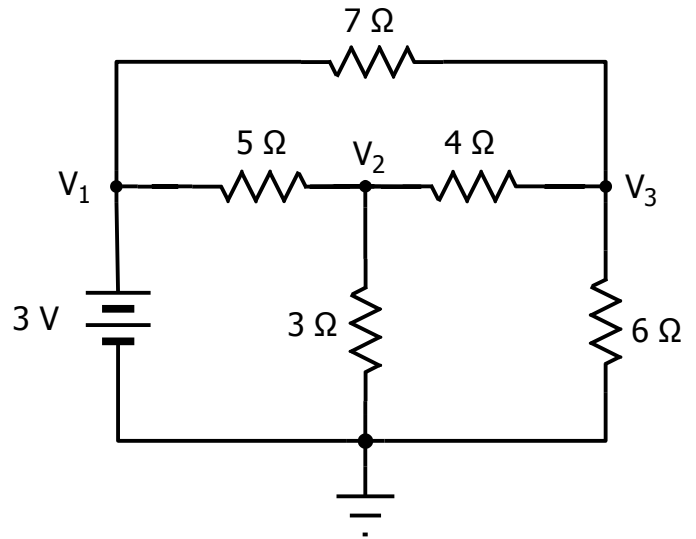


ECE3 Fall 2020  
Quiz 1

Name \_\_\_\_\_  
Family (Last) Name      Given (First) Name

1. Write (DO NOT SOLVE) the KCL equations for nodes  $V_2$  and  $V_3$ .

Because the textbooks teach KCL this way, you MUST assume that all currents are leaving node  $V_2$  when writing the KCL equation for  $V_2$ . Likewise for node  $V_3$ .



2. T F Pre-Labs are submitted one per team.