

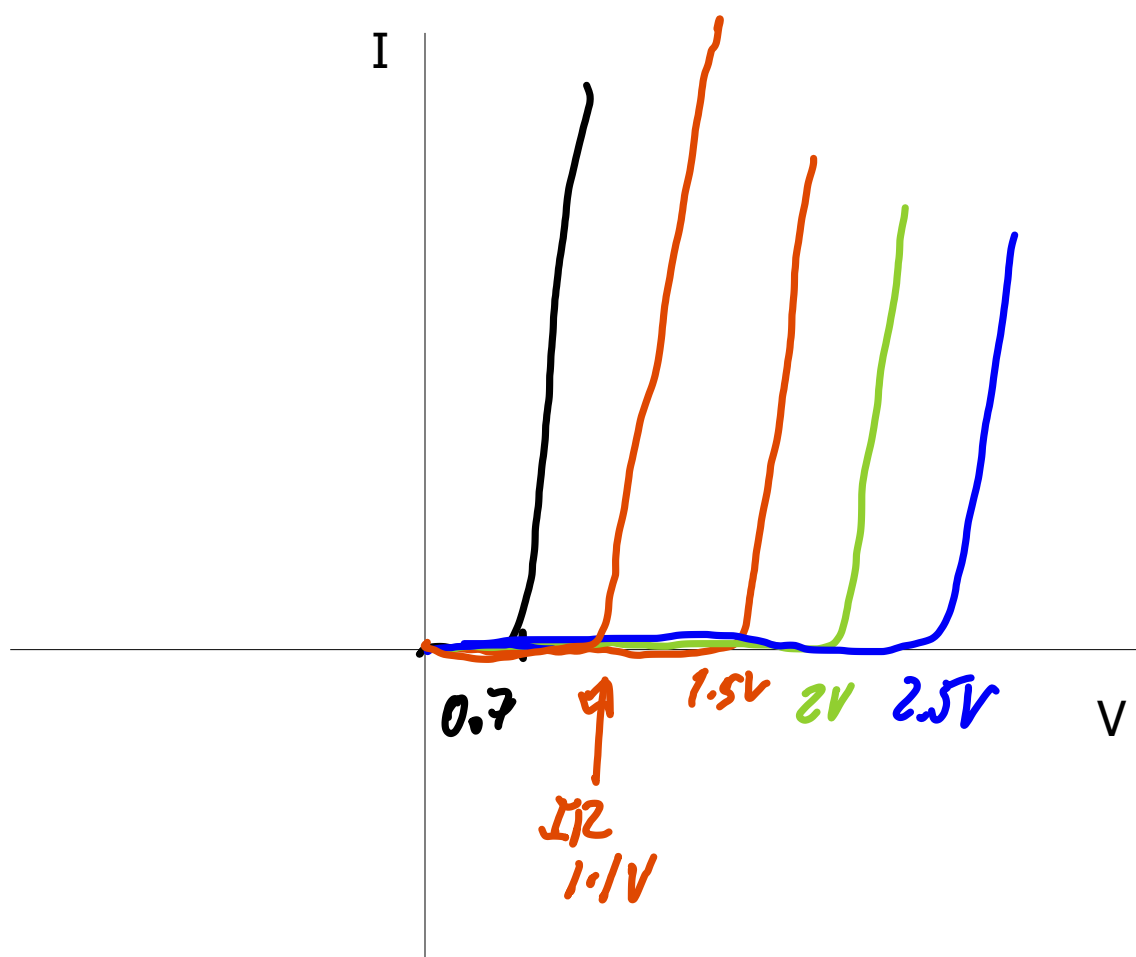


# LED I-V CURVE

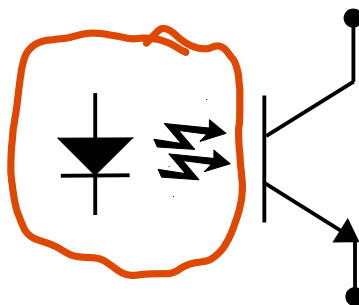

# PHOTOTRANSISTOR I-V CURVE

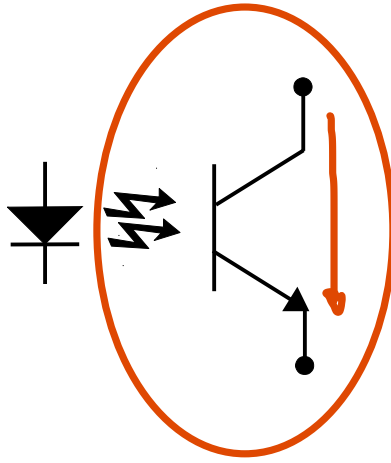

## TRANSIENTS

Transients occur everywhere!


- Ice cube tray
- Car accelerating from red light
- Oven warmup
- Response to Federal Reserve Interest Change
- Acceptance of social change

They non-zero response times to instantaneous changes.


Systems with transients are called Dynamical Systems. They have dynamics.

## CAPACITORS & INDUCTORS HAVE DYNAMICS

$$i(t) = C \frac{dv_c(t)}{dt}$$

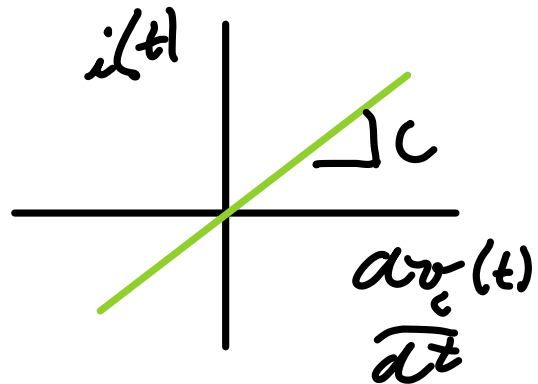


Water analogy:

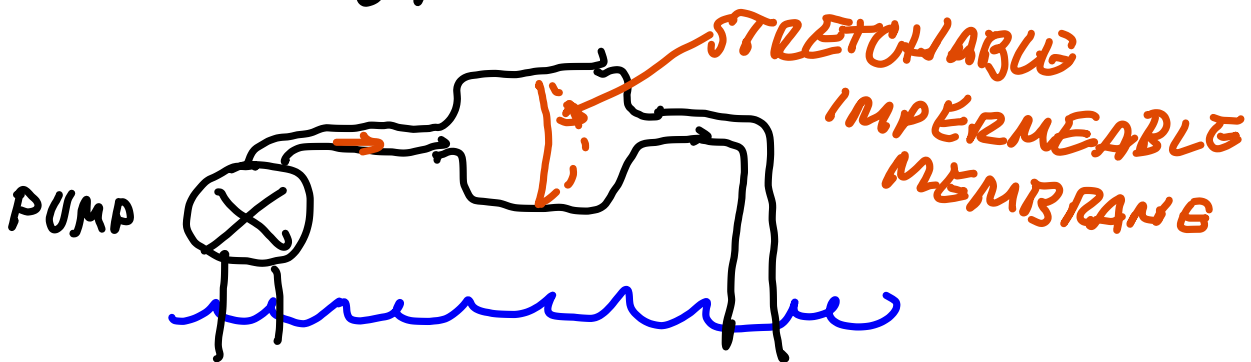

Pump forces water into tank, causing membrane to stretch. Membrane tries to force water back out of tank.

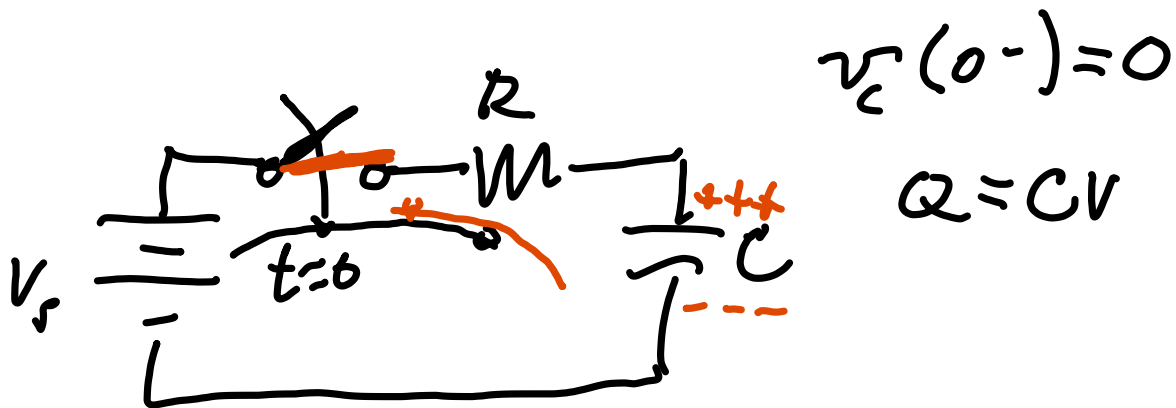
## ELECTRICAL VERSION OF WATER TANK MEMBRANE



As  $g \uparrow$ ,  $v_c \uparrow$  & pushes harder on carriers  
to move clockwise.  
When  $v_c = V_s$ , current stops.
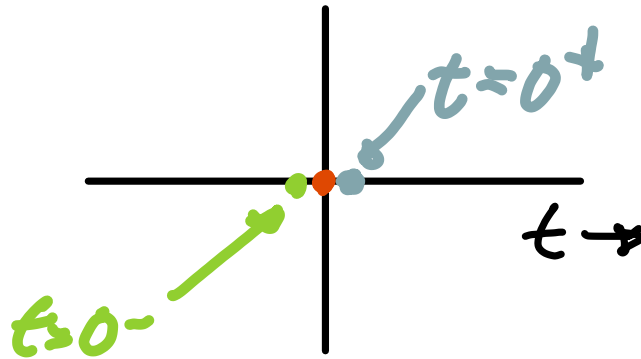
## CAPACITORS HATE CHANGE IN VOLTAGE

And will cause or allow any amount of current to prevent a change, at least for an infinitesimal amount of time.




$t=0^-$  to  $t=0^+$   
is important!

$$i_c = C \frac{dv_c(t)}{dt}$$

For a step change in  $v_c(t)$ , the cap acts like a short OR an ideal voltage source, for an infinitesimal amount of time. Whatever is needed to prevent a change in  $v_c$ .

$$v_c(0^+) = v_c(0^-)$$

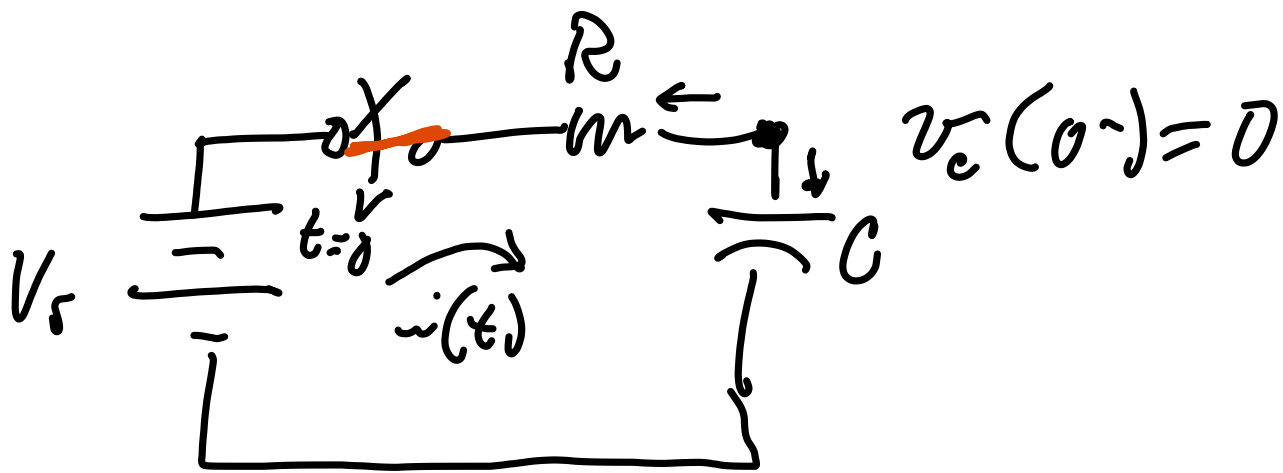

We want  $v_c(t)$ .

$$i_R(t) + i_C(t) = 0 \rightarrow \frac{v_R(t)}{R} + C \frac{dv_C(t)}{dt}$$

$$\frac{v_c - V_s}{R} + C \frac{dv_c(t)}{dt} = 0$$

$$\frac{dv_c}{dt} + \frac{1}{RC} v_c = \frac{V_s}{RC}$$



$$\frac{dv_c}{dt} + \frac{1}{RC} v_c = \frac{V_s}{RC} \quad P = \frac{1}{RC} \quad Q = \frac{V_s}{RC}$$

$$e^{\int_0^t P dx} = e^{\int_0^t \frac{1}{RC} dx} = e^{\frac{1}{RC} x} \Big|_0^t = e^{t/RC}$$

$$e^{t/RC} \frac{dv_c}{dt} + \frac{1}{RC} e^{t/RC} v_c = e^{t/RC} \frac{V_s}{RC}$$

$$\frac{d}{dt} (v_c e^{t/RC}) = e^{t/RC} \frac{V_s}{RC}$$


$$v_c e^{t/RC} = \frac{V_s}{RC} (RC) e^{t/RC} = V_s e^{t/RC} + C$$


$$v_c = V_s + C e^{-t/RC} \quad v_c(0^-) = 0 \Rightarrow$$

$$v_c(0^+) = V_s + C e^0 = 0 \quad v_c(0^+) = 0$$

$$C = -V_s$$
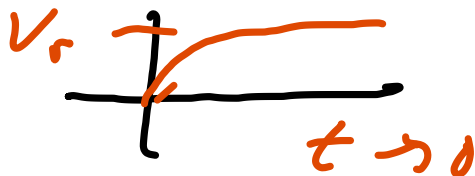
$$v_c(t) = V_s - V_s e^{-t/RC} = V_s (1 - e^{-t/RC})$$



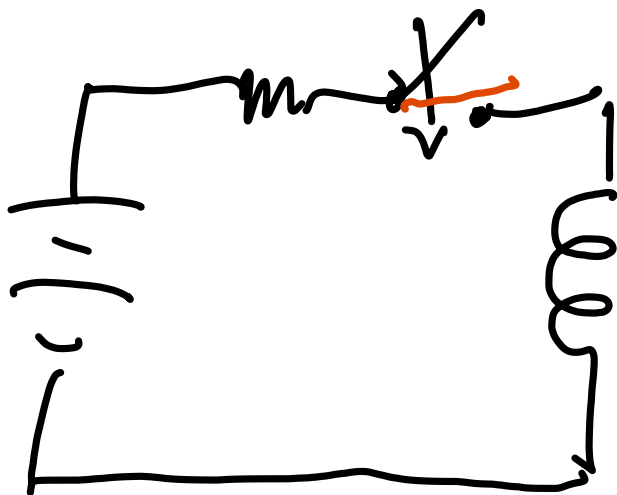

$$i(0^-) = 0$$

$$-V_s + iR + L \frac{di}{dt} = 0$$

## TIME CONSTANT

The time it takes for  $v_c(t)$  to complete 63.2% of its journey.

Symbol:  $\tau$  (lower case tau)

$$1 - \frac{1}{e} \approx 0.632$$

$$1 - e^{-t/RC} = 1 - \frac{1}{e^{t/RC}}; \text{ if } t = RC, 1 - \frac{1}{e}$$

LONG TIME:  $5\tau$  (all transients have died out)

